



Participant ID	2590138040307
Participant Name	KONNELLA DIVAKAR
Test Center Name	iON Digital Zone iDZ Sheela Nagar
Test Date	20/12/2025
Test Time	1:00 PM - 3:00 PM
Subject	Probationary Engineer Electronics

Section : General Aptitude

Q.1 If 30 workers earn ₹4,000 in 3 days, how much (in ₹) will 54 workers earn in 6 days?

- Ans
- ☒ A. ₹14,150
 - ☒ B. ₹13,900
 - ☒ C. ₹14,600
 - ☒ D. ₹14,400

Question ID : 441009523067
Option 1 ID : 4410092047689
Option 2 ID : 4410092047688
Option 3 ID : 4410092047690
Option 4 ID : 4410092047687
Status : Answered
Chosen Option : B

Adda247

Test Prime

ALL EXAMS, ONE SUBSCRIPTION



1,00,000+
Mock Tests



**Personalised
Report Card**



**Unlimited
Re-Attempt**



600+
Exam Covered



25,000+ Previous
Year Papers



500%
Refund



ATTEMPT FREE MOCK NOW

Q.2 During a sale, 44% of the goods are sold at a profit of 28%, 25% of the remaining goods are sold at a profit of 48%, and the rest are sold at a loss of 13%. All items have the same cost price. If there is an overall profit of x%, then what is the value of x?

- Ans
- ☒ A. 19.29
 - ☒ B. 15.38
 - ☒ C. 20.29
 - ☒ D. 13.58

Question ID : 441009547580
Option 1 ID : 4410092145717
Option 2 ID : 4410092145719
Option 3 ID : 4410092145718
Option 4 ID : 4410092145716
Status : Answered
Chosen Option : A

Q.3 A scooter travelling at two – third of its actual speed covers 60

- Ans
- ☒ A. 80 km/hr
 - ☒ B. 75 km/hr
 - ☒ C. 90 km/hr
 - ☒ D. 96 km/hr

Question ID : 441009543938
Option 1 ID : 4410092131151
Option 2 ID : 4410092131150
Option 3 ID : 4410092131148
Option 4 ID : 4410092131149
Status : Answered
Chosen Option : A

Q.4 X varies inversely as Y and Y varies inversely as Z. In a parti

- Ans
- ☒ A. 15
 - ☒ B. 16
 - ☒ C. 19
 - ☒ D. 17

Question ID : 441009898099
Option 1 ID : 4410093546467
Option 2 ID : 4410093546466
Option 3 ID : 4410093546469
Option 4 ID : 4410093546468
Status : Answered
Chosen Option : B

Q.5 The sum of two numbers is 49, and their LCM is 70. The two numbers are:

- Ans ☒ A. 19, 30
☒ B. 14, 35
☒ C. 12, 37
☒ D. 7, 42

Question ID : 441009525513
Option 1 ID : 4410092057473
Option 2 ID : 4410092057471
Option 3 ID : 4410092057472
Option 4 ID : 4410092057474
Status : Answered
Chosen Option : B

Q.6 The LCM of the numbers 18, 78 and 49 is:

- Ans ☒ A. 11466
☒ B. 11526
☒ C. 11486
☒ D. 11506

Question ID : 441009525651
Option 1 ID : 4410092058023
Option 2 ID : 4410092058024
Option 3 ID : 4410092058025
Option 4 ID : 4410092058026
Status : Answered
Chosen Option : C

Q.7 A class of 75 students took a Physics test. 22 students had an average score of 90. The other students had an average score of 70. What is the average score (rounded off to one decimal place) of the whole class?

- Ans ☒ A. 73.6
☒ B. 75.9
☒ C. 83.1
☒ D. 72.3

Question ID : 441009539529
Option 1 ID : 4410092113514
Option 2 ID : 4410092113512
Option 3 ID : 4410092113513
Option 4 ID : 4410092113515
Status : Answered
Chosen Option : B

Q.8 The ratio of the heights of a right circular cone and a right circular cylinder is 8 : 3, and the ratio of the radii of their bases is 9 : 2. If the volume of the cylinder is 792 cm³, then the volume (in cm³) of the cone is:

- Ans ☒ A. 14246
☒ B. 14256
☒ C. 14249
☒ D. 14257

Question ID : 441009600723
Option 1 ID : 4410092358010
Option 2 ID : 4410092358009
Option 3 ID : 4410092358011
Option 4 ID : 4410092358012
Status : Answered
Chosen Option : C

Q.9 The cost of a washing machine is 40% less than the cost of a TV. If the cost of the washing machine increases by 73% and that of the TV decreases by 67%, then what is the percentage change in the total cost of 5 washing machines and 2 TVs?

- Ans ☒ A. Decrease by 18%
☒ B. Decrease by 24%
☒ C. Increase by 17%
☒ D. Increase by 19%

Question ID : 441009560868
Option 1 ID : 4410092198740
Option 2 ID : 4410092198742
Option 3 ID : 4410092198739
Option 4 ID : 4410092198741
Status : Answered
Chosen Option : D

Q.10 During a Big Billion Day sale, a flagship mobile phone was available at a 20% discount on an e-commerce platform. Customers purchasing for the first time on the platform received an additional 10% cashback on the billing amount. Suraj, being a first-time user, purchased the mobile phone for ₹36,000. Find the original marked price (in ₹) of the mobile phone.

- Ans ☒ A. 49,500
☒ B. 45,000
☒ C. 50,000
☒ D. 48,500

Question ID : 441009545616
Option 1 ID : 4410092137862
Option 2 ID : 4410092137860
Option 3 ID : 4410092137863
Option 4 ID : 4410092137861
Status : Answered
Chosen Option : A

Q.11 Mohan has two grandsons, Pramod and Ashish. 14-year-old Pramod gets some money from Mohan's wealth, and 15-year-old Ashish gets the rest of the money. But Pramod and Ashish will get the money only when they turn 23 years old. Till then, the money is in a bank getting interest at the rate of 8% per annum, compounded annually. When both turn 23, they receive the same amount. How much (in ₹) had Mohan given Ashish initially, if the total money with Mohan was ₹24,700?

- Ans
- ☒ A. 11,625
 - ☒ B. 12,825
 - ☒ C. 13,175
 - ☒ D. 11,875

Question ID : 441009572920
Option 1 ID : 4410092246803
Option 2 ID : 4410092246800
Option 3 ID : 4410092246802
Option 4 ID : 4410092246801
Status : Answered
Chosen Option : B

Q.12 Sujit is three times as old as his son, and his daughter is 3 years younger than the son. If the sum of the ages of these three people 3 years ago was 63 years, then Sujit's present age (in years) is:

- Ans
- ☒ A. 85
 - ☒ B. 45
 - ☒ C. 36
 - ☒ D. 54

Question ID : 4410091220276
Option 1 ID : 4410094814528
Option 2 ID : 4410094814527
Option 3 ID : 4410094814529
Option 4 ID : 4410094814530
Status : Answered
Chosen Option : C

Section : Reasoning

Q.1 Each of the digits in the number 5976248 is arranged in descending order from left to right. The positions of how many digits will remain unchanged as compared to those in the original number?

- Ans
- ☒ A. Three
 - ☒ B. One
 - ☒ C. None
 - ☒ D. Two

Question ID : 441009585670
Option 1 ID : 4410092297809
Option 2 ID : 4410092297807
Option 3 ID : 4410092297806
Option 4 ID : 4410092297808
Status : Answered
Chosen Option : D

Q.2 What should come in place of ? in the given series based on the English alphabetical order?

DZD HWI LTN PQS ?

- Ans ☒ A. HGT
☒ B. DFR
☒ C. TNX
☒ D. BGF

Question ID : 4410091449739
Option 1 ID : 4410095727437
Option 2 ID : 4410095727438
Option 3 ID : 4410095727439
Option 4 ID : 4410095727436
Status : Answered
Chosen Option : C

Q.3 In a certain code language, 'SONG' is coded as '6423' and 'ONES' is coded as '2648'. How is 'E' coded in that language?

- Ans ☒ A. 2
☒ B. 6
☒ C. 4
☒ D. 8

Question ID : 441009149615
Option 1 ID : 441009594194
Option 2 ID : 441009594195
Option 3 ID : 441009594196
Option 4 ID : 441009594197
Status : Answered
Chosen Option : D

Q.4 Seven boxes, Q, R, S, T, G, H and I, are kept one over the other, but not necessarily in the same order.
Only H is kept above I. Only T is kept between S and Q. Only G is kept below S.
How many boxes are kept between R and G?

- Ans ☒ A. One
☒ B. Two
☒ C. None
☒ D. Three

Question ID : 441009149599
Option 1 ID : 441009594135
Option 2 ID : 441009594136
Option 3 ID : 441009594134
Option 4 ID : 441009594137
Status : Answered
Chosen Option : A

Q.5 Refer to the following letter and symbol series and answer the question that follows. Counting to be done from left to right only.

(Left) N Z \ D J J G % W C U B F E Q \ G V # C S (Right)

How many such symbols are there each of which is immediately preceded by a letter and also immediately followed by a symbol?

- Ans
- ☒ A. Three
 - ☒ B. None
 - ☒ C. Two
 - ☒ D. One

Question ID : 441009789414
Option 1 ID : 4410093111658
Option 2 ID : 4410093111655
Option 3 ID : 4410093111657
Option 4 ID : 4410093111656
Status : Answered
Chosen Option : D

Q.6 Based on the English alphabetical order, three of the following four letter-cluster pairs are alike in a certain way and thus form a group. Which letter-cluster pair DOES NOT belong to that group?
(Note: The odd one out is not based on the number of consonants/vowels or their position in the letter-cluster.)

- Ans
- ☒ A. TU-WX
 - ☒ B. CE-GI
 - ☒ C. EG-IK
 - ☒ D. JL-NP

Question ID : 441009782150
Option 1 ID : 4410093082603
Option 2 ID : 4410093082605
Option 3 ID : 4410093082606
Option 4 ID : 4410093082604
Status : Answered
Chosen Option : D

Q.7 Refer to the given letter series and answer the question that follows.
Counting to be done from left to right only.

(Left) Q C Y B H I N M K O P G D A W E D C T U I T (Right)

How many such consonants are there, each of which is immediately preceded by a vowel and also immediately followed by a vowel?

- Ans
- ☒ A. Two
 - ☒ B. More Than Two
 - ☒ C. None
 - ☒ D. One

Question ID : 441009797517
Option 1 ID : 4410093144069
Option 2 ID : 4410093144070
Option 3 ID : 4410093144067
Option 4 ID : 4410093144068
Status : Answered
Chosen Option : D

Q.8 LQ 22 is related to HN 5 in a certain way. In the same way, KR 19 is related to GO 2. To which of the following is GH 16 related, following the same logic?

- Ans
- ☒ A. CE -1
 - ☒ B. CD -5
 - ☒ C. BE -5
 - ☒ D. BD -1

Question ID : 441009787163
Option 1 ID : 4410093102652
Option 2 ID : 4410093102654
Option 3 ID : 4410093102653
Option 4 ID : 4410093102651
Status : Answered
Chosen Option : B

Q.9 Based on the English alphabetical order, three of the following four letter-clusters are alike in a certain way and thus form a group. Which letter-cluster DOES NOT belong to that group?
(Note: The odd one out is not based on the number of consonants/vowels or their position in the letter-cluster.)

- Ans
- ☒ A. RXT
 - ☒ B. NTP
 - ☒ C. LRM
 - ☒ D. PVR

Question ID : 441009774069
Option 1 ID : 4410093050282
Option 2 ID : 4410093050280
Option 3 ID : 4410093050279
Option 4 ID : 4410093050281
Status : Answered
Chosen Option : D

Q.10 Select the pair which follows the same pattern as that followed by the two sets of pairs given below. Both pairs follow the same pattern.

QPI : PMJ
DTN : CQO

- Ans ☒ A. RPI : QMI
☒ B. PMS : OJT
☒ C. MQE : LNE
☒ D. IMH : HII

Question ID : 441009777828
Option 1 ID : 4410093065318
Option 2 ID : 4410093065317
Option 3 ID : 4410093065315
Option 4 ID : 4410093065316
Status : Answered
Chosen Option : B

Q.11 Seven people F, G, H, I, V, W, and X are sitting in a straight line facing north. Only two people sit between G and W. Only X sits to the right of H. Only one person sits between W and H. I sits at some place to the right of F and at some place to the left of V. How many people sit between V and F?

- Ans ☒ A. Two
☒ B. One
☒ C. Four
☒ D. Three

Question ID : 441009787074
Option 1 ID : 4410093102296
Option 2 ID : 4410093102295
Option 3 ID : 4410093102298
Option 4 ID : 4410093102297
Status : Answered
Chosen Option : D

Q.12 Each vowel in the word MINDFUL is changed to the letter immediately following it in the English alphabetical order and each consonant is changed to the letter immediately preceding it in the English alphabetical order. How many vowels are there in the group of letters thus formed?

- Ans ☒ A. None
☒ B. Three
☒ C. One
☒ D. Two

Question ID : 441009798015
Option 1 ID : 4410093146059
Option 2 ID : 4410093146062
Option 3 ID : 4410093146060
Option 4 ID : 4410093146061
Status : Answered
Chosen Option : C

Q.13 What will come in place of the question mark (?) in the following equation, if '+' and '-' are interchanged and 'x' and '÷' are interchanged?

$4 \div 2 + 6 \times 3 - 4 = ? + 16$

- Ans ☒ A. 22
☒ B. 24
☒ C. 28
☒ D. 26

Question ID : 441009555516
Option 1 ID : 4410092177378
Option 2 ID : 4410092177379
Option 3 ID : 4410092177381
Option 4 ID : 4410092177380
Status : Answered
Chosen Option : D

Section : Question Based on Electronics Engineering

Q.1 The system has an impulse response defined by $h(t) = \sin(5t)$. Which of the following statements correctly describes the system?

- Ans ☒ A. System cannot be classified without the input signal.
☒ B. System is causal because $h(t)$ is defined for all t .
☒ C. The system is non-causal because $h(t)$ is non-zero for $t < 0$
☒ D. System is causal because $h(t)$ is always bounded between -1 and 1.

Question ID : 4410091529046
Option 1 ID : 4410096039298
Option 2 ID : 4410096039295
Option 3 ID : 4410096039296
Option 4 ID : 4410096039297
Status : Answered
Chosen Option : C

Q.2 Which of the following statements is correct in the context of the superheterodyne (SHD) receiver?

- S1: The intermediate frequency for FM radio in a SHD receiver is 455 kHz.
S2: The first section in a SHD receiver is frequency converter.
S3: The purpose of the RF section in a SHD receiver is to pick up the desired station.

- Ans ☒ A. S1 and S3 only
☒ B. S1, S2 and S3
☒ C. S1 and S2 only
☒ D. S3 only

Question ID : 4410091375839
Option 1 ID : 4410095434799
Option 2 ID : 4410095434800
Option 3 ID : 4410095434798
Option 4 ID : 4410095434797
Status : Answered
Chosen Option : C

Q.3 The charge neutrality condition in a semiconductor states that:

- Ans ☒ A. The net density of negative charges is less than the net density of positive charges.
- ☒ B. The net density of negative charges is equal to the net density of positive charges.
- ☒ C. The net density of negative charges is greater than the net density of positive charges.
- ☒ D. The net density of negative charges is always equal to zero.

Question ID : 44100929887
Option 1 ID : 441009119003
Option 2 ID : 441009119001
Option 3 ID : 441009119002
Option 4 ID : 441009119004
Status : Answered
Chosen Option : C

Q.4 A unity-feedback system has open-loop transfer function:


$$G(s)H(s) = \frac{K(s + 1)}{s^2 + 4s + 13}$$

What is the angle of arrival (in degrees) of the root locus at the zero $z = -1$?

- Ans ☒ A. 270°
- ☒ B. 90°
- ☒ C. 0°
- ☒ D. 180°

Question ID : 4410091454157
Option 1 ID : 4410095744944
Option 2 ID : 4410095744942
Option 3 ID : 4410095744941
Option 4 ID : 4410095744943
Status : Answered
Chosen Option : D

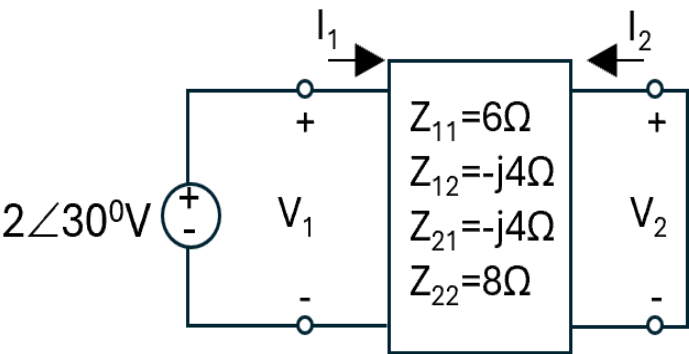Q.5 Consider the two-port network shown. Port 1 is excited by $V_1 = 2\angle 30^\circ \text{ V}$ and Port 2 is short-circuited ($V_2=0$). Determine the input current I_1 and the output current I_2 .



- Ans
- ☒ A. $I_1 = 0.25\angle(-30^\circ) \text{ A}$, $I_2 = 0.125\angle 60^\circ \text{ A}$
 - ☒ B. $I_1 = 0.25\angle 30^\circ \text{ A}$, $I_2 = 0.125\angle 120^\circ \text{ A}$
 - ☒ C. $I_1 = 0.333\angle 30^\circ \text{ A}$, $I_2 = 0$
 - ☒ D. $I_1 = 0.25\angle 30^\circ \text{ A}$, $I_2 = 0.125\angle(-60^\circ) \text{ A}$

Question ID : 4410091287476
Option 1 ID : 4410095081694
Option 2 ID : 4410095081691
Option 3 ID : 4410095081692
Option 4 ID : 4410095081693
Status : Answered
Chosen Option : A

Q.6 A series R–L–C circuit is excited by a sinusoidal source with frequency ω below its resonant frequency ω_0 . What is the nature of the circuit and the phase relationship between the supply voltage and the current?

- Ans
- ☒ A. Inductive circuit; current lags the voltage
 - ☒ B. Capacitive circuit; current leads the voltage
 - ☒ C. Purely resistive circuit; current is in phase with the voltage
 - ☒ D. Inductive circuit; current leads the voltage

Question ID : 4410091497633
Option 1 ID : 4410095915556
Option 2 ID : 4410095915557
Option 3 ID : 4410095915558
Option 4 ID : 4410095915559
Status : Answered
Chosen Option : C

Q.7 A silicon photodiode has a responsivity of 0.6 A/W at a certain wavelength. If the incident optical power is 2 milliwatts, then what is the photocurrent generated?

- Ans ☒ A. 0.6 μ A
☒ B. 1.2 mA
☒ C. 3.2 mA
☒ D. 1.2 μ A

Question ID : 4410091369258
Option 1 ID : 4410095408486
Option 2 ID : 4410095408488
Option 3 ID : 4410095408489
Option 4 ID : 4410095408487
Status : Answered
Chosen Option : D

Q.8 If a first-order low-pass active filter has a cut-off frequency of 2 KHz and a passband gain of 20, the gain (approximately) at frequency 2 KHz is _____.

- Ans ☒ A. 28
☒ B. 20
☒ C. 14
☒ D. 2

Question ID : 4410091367322
Option 1 ID : 4410095400741
Option 2 ID : 4410095400739
Option 3 ID : 4410095400740
Option 4 ID : 4410095400742
Status : Answered
Chosen Option : D

Q.9 Match the following columns with reference to various regions of operation of the MOS capacitor with p-substrate.

Regions of operation	Condition or validity
I- Accumulation	A- Gate voltage much greater than threshold voltage
II- Depletion	B- Gate voltage less than zero
III- Inversion	C- Gate voltage greater than zero but less than threshold voltage

- Ans ☒ A. I-A II- B III- C
☒ B. I-A II- C III- B
☒ C. I-C II- B III- A
☒ D. I-B II- C III- A

Question ID : 4410091369218
Option 1 ID : 4410095408329
Option 2 ID : 4410095408326
Option 3 ID : 4410095408328
Option 4 ID : 4410095408327
Status : Answered
Chosen Option : C

Q.10 A PAL can implement functions in sum-of-products form. For the Boolean function: $F(A,B,C,D)=\sum m(0,1,2,4,5,6,8,9,10,12,13,14)$ What is the minimum number of product terms required to implement F using a PAL, after Karnaugh map minimization?

- Ans
- ☒ A. 4
 - ☒ B. 1
 - ☒ C. 2
 - ☒ D. 3

Question ID : 4410091521391
Option 1 ID : 4410096008675
Option 2 ID : 4410096008672
Option 3 ID : 4410096008673
Option 4 ID : 4410096008674
Status : Answered
Chosen Option : D

Q.11 Which of the given statements is/are correct in the context of a direct coupling in a multistage amplifier?

- S1:** Direct coupling is suited for amplifying AC signals with frequencies as a fraction of hertz.
S2: It can amplify direct current as a DC amplifier.
S3: Q point of the BJT in a direct coupling multistage amplifier is not affected by the temperature variation.

- Ans
- ☒ A. S1, S2 and S3
 - ☒ B. S1 and S3 only
 - ☒ C. S1 and S2 only
 - ☒ D. S2 and S3 only

Question ID : 4410091371691
Option 1 ID : 4410095418163
Option 2 ID : 4410095418162
Option 3 ID : 4410095418160
Option 4 ID : 4410095418161
Status : Answered
Chosen Option : D

Q.12 Which of the following statements is correct in the context of the AM envelope detector circuit?

- S1: It is suitable only if the modulation index is > 1 .
S2: It works only if the carrier is present.
S3: It is a type of synchronous detector.

- Ans ☒ A. Only S2 and S3
☒ B. Only S1 and S3
☒ C. Only S2
☒ D. S1 and S2 only

Question ID : 4410091372212
Option 1 ID : 4410095420264
Option 2 ID : 4410095420263
Option 3 ID : 4410095420262
Option 4 ID : 4410095420265
Status : Answered
Chosen Option : B

Q.13 What is the typical current profile of a TTL output driver when switching from low to high?

- Ans ☒ A. Current spikes up as the output switches and then gradually decreases.
☒ B. No current is drawn during the transition.
☒ C. Current remains constant throughout the transition.
☒ D. The current first decreases, then increases.

Question ID : 44100997293
Option 1 ID : 441009387175
Option 2 ID : 441009387177
Option 3 ID : 441009387176
Option 4 ID : 441009387178
Status : Answered
Chosen Option : A

Q.14 For a certain sequence detector, the designer uses a Mealy FSM instead of a Moore FSM. What is the most likely reason for this choice?

- Ans ☒ A. The detector requires faster output response upon input pattern recognition.
☒ B. The detector needs to minimise power.
☒ C. Moore FSMs cannot detect input sequences.
☒ D. The machine produce output only after the entire sequence is detected.

Question ID : 4410091521103
Option 1 ID : 4410096007595
Option 2 ID : 4410096007594
Option 3 ID : 4410096007597
Option 4 ID : 4410096007596
Status : Answered
Chosen Option : A

Q.15 Which of the following options is correct for a modulated signal $s(t) = e^{-at} \cos [(w_c + \Delta w) t] u(t)$, where a , w_c and Δw are non-negative constant? Assume $w_c \gg \Delta$.

- Ans ☒ A. Complex envelope of $S(t)$ is $e^{-at} u(t) e^{-j\Delta wt}$
☒ B. Complex envelope of $S(t)$ is $e^{-at} u(t) e^{j\Delta wt}$
☒ C. Complex envelope of $S(t)$ is $e^{-at} u(t) e^{-j\Delta wt}$
☒ D. Complex envelope of $S(t)$ is $e^{-at} u(t) e^{j\Delta wt}$

Question ID : 4410091379408
Option 1 ID : 4410095449053
Option 2 ID : 4410095449050
Option 3 ID : 4410095449052
Option 4 ID : 4410095449051
Status : Answered
Chosen Option : A

Q.16 At absolute zero temperature (0 K), an intrinsic semiconductor behaves as a/an _____ and has ideally _____.

- Ans ☒ A. Insulator, infinite resistivity
☒ B. Conductor, infinite resistivity
☒ C. Conductor, zero resistivity
☒ D. Insulator, zero resistivity

Question ID : 4410091506604
Option 1 ID : 4410095950774
Option 2 ID : 4410095950773
Option 3 ID : 4410095950771
Option 4 ID : 4410095950772
Status : Answered
Chosen Option : C

Q.17 A digital filter is required to satisfy the following specifications:
a) Exactly linear phase
b) Sharp transition band
c) Stable response even if coefficient quantization occurs
Which of the given filter architecture is the most appropriate?

- Ans ☒ A. Direct-form IIR Chebyshev Type-I filter
☒ B. Long-length optimal equiripple FIR filter
☒ C. Long-length FIR filter using rectangular window
☒ D. Cascade-form IIR elliptic filter

Question ID : 4410091525681
Option 1 ID : 4410096025891
Option 2 ID : 4410096025892
Option 3 ID : 4410096025890
Option 4 ID : 4410096025893
Status : Answered
Chosen Option : A

Q.18 If a continuous-time signal $x(t)$ has non-zero continuous spectrum only for $f \leq 3 \text{ kHz}$ what happens if it is sampled at $f_s = 5 \text{ kHz}$?

- Ans
- ☒ A. Oversampling
 - ☒ B. Perfect reconstruction of the signal
 - ☒ C. Undersampling and aliasing
 - ☒ D. Time scaling

Question ID : 4410091408437
Option 1 ID : 4410095562710
Option 2 ID : 4410095562709
Option 3 ID : 4410095562712
Option 4 ID : 4410095562711
Status : Answered
Chosen Option : C

Q.19 Which of the following is the key characteristic of a Field-Programmable Gate Array (FPGA) that distinguishes it from a Complex Programmable Logic Device (CPLD) in terms of architecture?

- Ans
- ☒ A. FPGAs are primarily used for implementing simple, fast logic, while CPLDs are used for complex, multi-core designs.
 - ☒ B. FPGAs typically have a coarse-grained, logic-block based architecture, while CPLDs have a fine-grained, array-based architecture.
 - ☒ C. FPGAs use a hierarchy of configurable logic blocks and programmable routing, whereas CPLDs use a single, large programmable AND-OR plane.
 - ☒ D. FPGAs use an array of interconnected macrocells, while CPLDs use Look-Up Tables (LUTs).

Question ID : 4410091265947
Option 1 ID : 4410094996668
Option 2 ID : 4410094996667
Option 3 ID : 4410094996669
Option 4 ID : 4410094996666
Status : Answered
Chosen Option : C

Q.20 A solid sphere of radius R has a volume charge density given by:

$$\rho_v(r) = \rho_0 \left(1 - \frac{r}{R}\right), \quad 0 \leq r \leq R,$$

where r is the distance from the center. What is the total charge Q of the sphere?

- Ans
- ☒ A. $(\pi / 6) \rho_0 R^3$
 - ☒ B. $(\pi / 2) \rho_0 R^3$
 - ☒ C. $(\pi / 12) \rho_0 R^3$
 - ☒ D. $(\pi / 3) \rho_0 R^3$

Question ID : 4410091455448
Option 1 ID : 4410095750092
Option 2 ID : 4410095750094
Option 3 ID : 4410095750091
Option 4 ID : 4410095750093
Status : Answered
Chosen Option : B

Q.21 Two perfect dielectric media are separated by a charge-free planar boundary. Their relative permittivities are: $\epsilon_{r1} = 6$, $\epsilon_{r2} = 2$. In medium 1, the electric field at a point P has magnitude $E_1 = 100$ V/m and makes an angle $\alpha_1 = 60^\circ$ with the normal to the boundary. Under electrostatic conditions, the angle α_2 in medium 2 and the magnitude E_2 are _____.

- Ans
- ☒ A. $\alpha_2 = 45^\circ$, $|E_2| = 100\sqrt{3}$ V/m
 - ☒ B. $\alpha_2 = 45^\circ$, $|E_2| = 100/3$ V/m
 - ☒ C. $\alpha_2 = 30^\circ$, $|E_2| = 100\sqrt{3}$ V/m
 - ☒ D. $\alpha_2 = 30^\circ$, $|E_2| = 100/3$ V/m

Question ID : 4410091525028

Option 1 ID : 4410096023313

Option 2 ID : 4410096023314

Option 3 ID : 4410096023311

Option 4 ID : 4410096023312

Status : Answered

Chosen Option : B

Q.22 If $x_1[n] \leftrightarrow X_1(z)$ and $x_2[n] \leftrightarrow X_2(z)$, then for $y[n] = 3x_1[n] - 2x_2[n]$, the Z-transform is:

- Ans
- ☒ A. $Y(z) = X_1(z) \cdot X_2(z)$
 - ☒ B. $Y(z) = 3X_1(z) - 2X_2(z)$
 - ☒ C. $Y(z) = X_1(z) + X_2(z)$
 - ☒ D. $Y(z) = 3X_1(z) \cdot X_2(z)$

Question ID : 4410091287552

Option 1 ID : 4410095081996

Option 2 ID : 4410095081995

Option 3 ID : 4410095081997

Option 4 ID : 4410095081998

Status : Answered

Chosen Option : B

Q.23 A single-stage common-emitter amplifier is modelled with h-parameters, $h_{ie} = 1000 \Omega$, $h_{fe} = 50$, and h_{re} is negligible. The collector resistor is $R_c = 4.7 \text{ K}\Omega$ and the amplifier drives a load $R_L = 10 \text{ K}\Omega$ connected at the collector (i.e., collector sees in parallel with R_L). Neglect h_{oe} effects. The

approximate midband voltage gain $A_v = \frac{V_o}{V_i}$ is:

- Ans
- ☒ A. -160
 - ☒ B. -200
 - ☒ C. -80
 - ☒ D. -120

Question ID : 4410091268877

Option 1 ID : 4410095008025

Option 2 ID : 4410095008027

Option 3 ID : 4410095008024

Option 4 ID : 4410095008026

Status : Answered

Chosen Option : D

Q.24 In weakly stationary process, _____.

- Ans ☒ A. mean value is dependent of the shift of time origin
- ☒ B. autocorrelation function dependent on the shift of time origin
- ☒ C. wide-sense stationary process and weakly stationary process are not same
- ☒ D. mean value is constant

Question ID : 4410091510031
Option 1 ID : 4410095964800
Option 2 ID : 4410095964802
Option 3 ID : 4410095964803
Option 4 ID : 4410095964801
Status : Answered
Chosen Option : B

Q.25 The junction (transition) capacitance of the PN junction exists in _____ bias and it is _____ proportional to the width of the barrier.

- Ans ☒ A. forward, inversely
- ☒ B. reverse, inversely
- ☒ C. forward, directly
- ☒ D. reverse, directly

Question ID : 4410091506530
Option 1 ID : 4410095950476
Option 2 ID : 4410095950477
Option 3 ID : 4410095950475
Option 4 ID : 4410095950478
Status : Answered
Chosen Option : B

Q.26 A 12-bit ADC with a full-scale range of 0 to 4.095 V receives an analog input of 2.5V. What is the corresponding digital output code in decimal form?

- Ans ☒ A. 1250
- ☒ B. 3000
- ☒ C. 2500
- ☒ D. 2000

Question ID : 4410091520936
Option 1 ID : 4410096006952
Option 2 ID : 4410096006953
Option 3 ID : 4410096006951
Option 4 ID : 4410096006950
Status : Answered
Chosen Option : A

Q.27 Determine the wavelength of the light emitted by a LED if the frequency of operation for the LED is 400 THz.

- Ans ☒ A. 500 nm
☒ B. 600 nm
☒ C. 1000 nm
☒ D. 750 nm

Question ID : 44100929801
Option 1 ID : 441009118664
Option 2 ID : 441009118662
Option 3 ID : 441009118663
Option 4 ID : 441009118661
Status : Answered
Chosen Option : A

Q.28 The electric potential in a region is given by:
 $V(x, y, z) = 2x + 3y^2 - 4z$ volts.
At the point P(1, -1, 2), find the electric field vector $\mathbf{E}(P)$ in unit vector form ($\mathbf{a}_x, \mathbf{a}_y, \mathbf{a}_z$).

- Ans ☒ A. $-2 \mathbf{a}_x - 6 \mathbf{a}_y + 4 \mathbf{a}_z$ V/m
☒ B. $-2 \mathbf{a}_x + 6 \mathbf{a}_y + 4 \mathbf{a}_z$ V/m
☒ C. $-2 \mathbf{a}_x + 6 \mathbf{a}_y - 4 \mathbf{a}_z$ V/m
☒ D. $+2 \mathbf{a}_x - 6 \mathbf{a}_y - 4 \mathbf{a}_z$ V/m

Question ID : 4410091455476
Option 1 ID : 4410095750211
Option 2 ID : 4410095750212
Option 3 ID : 4410095750214
Option 4 ID : 4410095750213
Status : Answered
Chosen Option : A

Q.29 What is the result of a 4-bit ring counter which performs left shifting the 4-bit number 0100 three times to the left?

- Ans ☒ A. 0010
☒ B. 0100
☒ C. 1000
☒ D. 0001

Question ID : 4410091521427
Option 1 ID : 4410096008812
Option 2 ID : 4410096008815
Option 3 ID : 4410096008814
Option 4 ID : 4410096008813
Status : Answered
Chosen Option : B

Q.30 An anti-causal discrete time system has the system function as $H(z) = \frac{2}{(1 - 0.4z^{-1})(1 - 1.1z^{-1})}$. The system is _____.

- Ans ☒ A. unstable because ROC does not include the unit circle
- ☐ B. stable because ROC is inside the smallest magnitude pole
- ☐ C. always stable because ROC: $|z| > 0.4$
- ☐ D. always unstable because ROC: $|z| > 1.1$

Question ID : 4410091529034
Option 1 ID : 4410096039249
Option 2 ID : 4410096039250
Option 3 ID : 4410096039247
Option 4 ID : 4410096039248
Status : Answered
Chosen Option : C

Q.31 In unsigned multiplication of two 6-bit numbers, what is the maximum bit-length of the output?

- Ans ☐ A. 7
- ☐ B. 11
- ☐ C. 6
- ☒ D. 12

Question ID : 4410091521378
Option 1 ID : 4410096008621
Option 2 ID : 4410096008622
Option 3 ID : 4410096008620
Option 4 ID : 4410096008623
Status : Answered
Chosen Option : D

Q.32 In a region of space, the magnetic field intensity is given by:
 $H(x, y, z) = y a_x - x a_y$
Find the total current I flowing through the square surface in the xy -plane bounded by $x = 0$, $x = 1$, $y = 0$, and $y = 1$. Assume the standard orientation: surface normal $a_n = a_z$ (counter-clockwise boundary when viewed from $+z$).

- Ans ☐ A. -1 A
- ☒ B. -2 A
- ☐ C. +2 A
- ☐ D. 0 A

Question ID : 4410091455528
Option 1 ID : 4410095750429
Option 2 ID : 4410095750430
Option 3 ID : 4410095750428
Option 4 ID : 4410095750427
Status : Answered
Chosen Option : D

Q.33 A medium has $\epsilon_r = 60$, $\mu_r = 1$, $\sigma = 3 \text{ S/m}$.
Let f_c be the frequency at which the conduction current density equals the displacement current density, i.e. $J_c = J_d$. Using the rule of ten, where the higher frequency is 10 times f_c and the lower frequency is $f_c / 10$, estimate the frequency ranges in which the medium behaves as a good conductor and as a good dielectric.

- Ans
- ☒ A. Good conductor: $f \leq 1 \text{ MHz}$; Good dielectric: $f \geq 100 \text{ MHz}$
 - ☒ B. Good conductor: $f \leq 9 \text{ MHz}$; Good dielectric: $f \geq 900 \text{ MHz}$
 - ☒ C. Good conductor: $f \leq 900 \text{ MHz}$; Good dielectric: $f \geq 90 \text{ GHz}$
 - ☒ D. Good conductor: $f \leq 90 \text{ MHz}$; Good dielectric: $f \geq 9 \text{ GHz}$

Question ID : 4410091455695
Option 1 ID : 4410095751106
Option 2 ID : 4410095751105
Option 3 ID : 4410095751104
Option 4 ID : 4410095751103
Status : Answered
Chosen Option : A

Q.34 A transistor in common-emitter configuration is described by the small-signal h-parameters $h_{ie} = 1 \text{ k}\Omega$, $h_{fe} = 100$, $h_{re} \approx 0$, and $h_{oe} \approx 0$. A sinusoidal signal source of amplitude $v_s = 0.20 \text{ V}$ with source resistance $R_s = 1 \text{ k}\Omega$ is connected between the base and emitter. Using the hybrid small-signal model based on these h-parameters, determine the amplitude of the small-signal collector current i_c . Select the correct option.

- Ans
- ☒ A. 20 mA
 - ☒ B. 10 mA
 - ☒ C. 50 mA
 - ☒ D. 5 mA

Question ID : 4410091525816
Option 1 ID : 4410096026416
Option 2 ID : 4410096026415
Option 3 ID : 4410096026417
Option 4 ID : 4410096026414
Status : Answered
Chosen Option : A

Q.35 A slab of perfect dielectric ($\epsilon_r = 2$) is adjacent to air. Inside the slab, the normal electric field is sinusoidal: $E_d(t) = E_0 \cos(\omega t) \mathbf{a}_n$, with $E_0 = 300$ V/m. Assume $\mu_r = 1$, no free surface charge at the interface, and the field is normal to the surface. Which option correctly gives the amplitudes of the displacement current density J_d in the dielectric and in air, respectively?

- Ans ☒ A. Both are zero
☒ B. Air value is twice the dielectric value
☒ C. Equal and non-zero (same value in both media)
☒ D. Dielectric value is twice the air value

Question ID : 4410091455626

Option 1 ID : 4410095750826

Option 2 ID : 4410095750825

Option 3 ID : 4410095750823

Option 4 ID : 4410095750824

Status : Answered

Chosen Option : A

Q.36 An AWGN channel operating at a large signal to noise ratio ($SNR \gg 1$) and bandwidth F has capacity C . If the signal to noise is quadrupled keeping F constant, then the resulting capacity of the channel C_1 is _____.

- Ans ☒ A. $C_1 = 4C$
☒ B. $C_1 = C + 2F$
☒ C. $C_1 = C + F$
☒ D. $C_1 = 2C$

Question ID : 4410091375850

Option 1 ID : 4410095434843

Option 2 ID : 4410095434841

Option 3 ID : 4410095434842

Option 4 ID : 4410095434844

Status : Answered

Chosen Option : B

Q.37 The corresponding minterm Boolean expression for 4-variable inputs A, B, C , and D , using the minterms m_3, m_4 , and m_7 , is _____.

- Ans ☒ A. $Y = \overline{A}\overline{B}CD + \overline{A}B\overline{C}D + \overline{A}BCD$
☒ B. $Y = \overline{A}BCD + \overline{A}B\overline{C}D + \overline{A}BCD$
☒ C. $Y = \overline{A}BCD + \overline{A}B\overline{C}D + \overline{A}BCD$
☒ D. $Y = \overline{A}BCD + \overline{A}BCD + \overline{A}BCD$

Question ID : 4410091533080

Option 1 ID : 4410096055279

Option 2 ID : 4410096055278

Option 3 ID : 4410096055280

Option 4 ID : 4410096055281

Status : Answered

Chosen Option : C

Q.38 In a synchronous binary counter, what is the primary characteristic that distinguishes it from an asynchronous counter?

- Ans ☒ A. The ability to count in decimal.
- ☒ B. All flip-flops are clocked simultaneously.
- ☒ C. The use of fewer flip-flops.
- ☒ D. Lower power consumption.

Question ID : 44100997357
Option 1 ID : 441009387436
Option 2 ID : 441009387437
Option 3 ID : 441009387435
Option 4 ID : 441009387438
Status : Answered
Chosen Option : B

Q.39 The system is described by the equation, $y(t) = x(t) + 3x(t - 1)$. The system is _____.

- Ans ☒ A. Causal and stable
- ☒ B. Causal but unstable
- ☒ C. Non-causal but stable
- ☒ D. Unstable and non-causal

Question ID : 4410091401048
Option 1 ID : 4410095533739
Option 2 ID : 4410095533740
Option 3 ID : 4410095533737
Option 4 ID : 4410095533738
Status : Answered
Chosen Option : A

Q.40 Which of the following statements is/are correct in the context of the encoding in a PCM system?

S1: A signal sampled at 8kHz in to 256 quantisation levels is encoded with 8 bits/sample.
S2: The basic function of an encoder in PCM is to convert quantised signal into a binary code sequence.
S3: The number of quantisation levels does not affect the encoding in a PCM system.

- Ans ☒ A. S3 and S2 only
- ☒ B. S1 and S3 only
- ☒ C. S1, S2 and S3
- ☒ D. S1 and S2 only

Question ID : 4410091376288
Option 1 ID : 4410095436714
Option 2 ID : 4410095436713
Option 3 ID : 4410095436715
Option 4 ID : 4410095436712
Status : Answered
Chosen Option : A

Q.41 Choose the correct statement for the encoding in a Pulse Code Modulation system?

S1: A signal sampled at 4kHz in to 32 quantization levels is encoded with 5 bits/sample.

S2: The basic function of an encoder is to convert quantized signal into a binary code sequence.

S3: The number of quantization levels does affect the encoding in Pulse Code Modulation system.

Ans ☒ A. S2 and S3 only

☒ B. S1 and S3 only

☒ C. S1, S2 and S3

☒ D. S1 and S2 only

Question ID : 4410091510129

Option 1 ID : 4410095965051

Option 2 ID : 4410095965050

Option 3 ID : 4410095965048

Option 4 ID : 4410095965049

Status : Answered

Chosen Option : C

Q.42 A semi-infinite transmission line supports only a forward-traveling wave.

$V(z) = V^+ e^{-\gamma z}$, $I(z) = (V^+ / Z_0) e^{-\gamma z}$.

The line has $Z_0 = 25 \Omega$ and propagation constant

$\gamma = \alpha + j\beta = \frac{\ln 2}{5} + j \frac{\pi}{15}$ per meter.

If the input voltage at $z = 0$ is $V(0) = 50 \angle 0^\circ$ V, find the current at $z = 5$ m.

Ans ☒ A. $2 \angle 0^\circ$ A

☒ B. $1 \angle +60^\circ$ A

☒ C. $2 \angle -60^\circ$ A

☒ D. $1 \angle -60^\circ$ A

Question ID : 4410091455793

Option 1 ID : 4410095751510

Option 2 ID : 4410095751509

Option 3 ID : 4410095751507

Option 4 ID : 4410095751508

Status : Answered

Chosen Option : C

Q.43 The small signal equivalent of a Zener diode in reverse breakdown region is represented by ____.

- Ans
- ☒ A. series combination of a DC current source and dynamic capacitance
 - ☒ B. shunt combination of a DC current source and dynamic inductance
 - ☒ C. shunt combination of a DC voltage source and dynamic inductance
 - ☒ D. series combination of a DC voltage source and small dynamic resistance

Question ID : 4410091506539
Option 1 ID : 4410095950512
Option 2 ID : 4410095950511
Option 3 ID : 4410095950513
Option 4 ID : 4410095950514
Status : Answered
Chosen Option : A

Q.44 A metal oxide semiconductor field effect transistor (MOSFET) is used in a self-biasing circuit with a drain resistor (R_D) and a source resistor (R_S). If the value R_S is increased, which of the following options is an immediate effect on the quiescent drain current (I_{DQ}) and the quiescent gate-source voltage (V_{GSQ})?

- Ans
- ☒ A. I_{DQ} decreases, and V_{GSQ} becomes more negative.
 - ☒ B. I_{DQ} increases, and V_{GSQ} increases.
 - ☒ C. I_{DQ} decreases, and V_{GSQ} becomes more positive.
 - ☒ D. I_{DQ} increases, and V_{GSQ} decreases.

Question ID : 4410091183763
Option 1 ID : 4410094669131
Option 2 ID : 4410094669129
Option 3 ID : 4410094669132
Option 4 ID : 4410094669130
Status : Answered
Chosen Option : C

Q.45 For a fixed (analog) spectrum continuous time signal $x(t)$, increasing the DFT frequency samples corresponds to ____ in the time domain.

- Ans
- ☒ A. zero-padding
 - ☒ B. circular time shift
 - ☒ C. time-scaling
 - ☒ D. signal compression

Question ID : 4410091525668
Option 1 ID : 4410096025839
Option 2 ID : 4410096025840
Option 3 ID : 4410096025838
Option 4 ID : 4410096025841
Status : Answered
Chosen Option : B

Q.46 An AC circuit has a voltage $v(t) = 30 \sin(\omega t + 80^\circ)$ V and a current $i(t) = 10 \sin(\omega t + 50^\circ)$ A. What are the apparent power (S) and reactive power (Q) of the circuit, respectively?

- Ans ☒ A. $S = 150$ VA, $Q = 75$ VAR
☒ B. $S = 100$ VA, $Q = 50$ VAR
☒ C. $S = 150\sqrt{2}$ VA, $Q = 150$ VAR
☒ D. $S = 150$ VA, $Q = 75\sqrt{3}$ VAR


Question ID : 4410091497644
Option 1 ID : 4410095915602
Option 2 ID : 4410095915603
Option 3 ID : 4410095915600
Option 4 ID : 4410095915601
Status : Answered
Chosen Option : B

Q.47 Choose the correct statement.
S1: The intermediate frequency for AM radio in superheterodyne (SHD) receiver is 455 kHz.
S2: The first section in a superheterodyne (SHD) receiver is frequency converter.
S3: The purpose of RF section in a superheterodyne (SHD) receiver is to picks up the desired station.

- Ans ☒ A. S1 and S2 only.
☒ B. S1, S2 and S3.
☒ C. S2 and S3 only.
☒ D. S1 and S3 only.

Question ID : 4410091510058
Option 1 ID : 4410095964904
Option 2 ID : 4410095964906
Option 3 ID : 4410095964907
Option 4 ID : 4410095964905
Status : Answered
Chosen Option : C

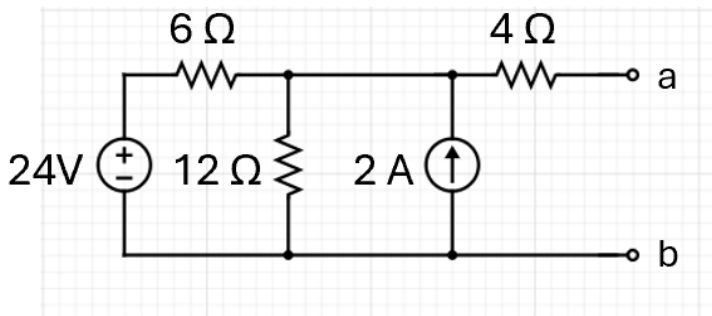Q.48 A load resistor R_L is to be connected across a–b in the given circuit. For maximum power transfer to R_L , find the value of R_L and the maximum power delivered to it.



- Ans
- ☒ A. $R_L = 8\ \Omega$, $P_{\max} = 12\ \text{W}$
 - ☒ B. $R_L = 8\ \Omega$, $P_{\max} = 18\ \text{W}$
 - ☒ C. $R_L = 6\ \Omega$, $P_{\max} = 24\ \text{W}$
 - ☒ D. $R_L = 4\ \Omega$, $P_{\max} = 36\ \text{W}$

Question ID : 4410091497985
Option 1 ID : 4410095917007
Option 2 ID : 4410095917005
Option 3 ID : 4410095917004
Option 4 ID : 4410095917006
Status : Answered
Chosen Option : D

Q.49 Which of the given statements is/are correct in the context of a voltage-controlled oscillator?

- S1:** It is an oscillator whose frequency can be changed by a variable DC voltage.
S2: Voltage-controlled oscillator can produce a non-sinusoidal output only.
S3: Voltage-controlled sawtooth oscillator cannot be designed using UJT.

- Ans
- ☒ A. S1, S2 and S3
 - ☒ B. Only S1 and S3
 - ☒ C. Only S2 and S3
 - ☒ D. Only S1

Question ID : 4410091367379
Option 1 ID : 4410095400963
Option 2 ID : 4410095400964
Option 3 ID : 4410095400962
Option 4 ID : 4410095400961
Status : Answered
Chosen Option : D

Q.50 A unity negative-feedback system has an open-loop transfer function:

$$G(s) = \frac{K(s + z)}{s^2(s + a)}, \text{ where } K > 0.$$

It is given that the system is unstable for every $K > 0$. A pure derivative controller with transfer function $G_c(s) = s$ is introduced in the forward path. Determine for which values of K the compensated system is stable. Assuming $a, z > 0$.

- Ans
- ☒ A. $K > 1/5$
 - ☒ B. $0 < K < 2$
 - ☒ C. $K > 0$
 - ☒ D. The system cannot be stabilized by a D-only controller

Question ID : 4410091451095

Option 1 ID : 4410095732848

Option 2 ID : 4410095732849

Option 3 ID : 4410095732850

Option 4 ID : 4410095732851

Status : Answered

Chosen Option : B

Q.51 Let $x(t)$ be a causal signal with Laplace transform $X(s)$. What is the Laplace transform of integral of $x(t)$?

- Ans
- ☒ A. $(X(s) - x(0))/s^2$
 - ☒ B. $X(s)/s^2$
 - ☒ C. $X(s)/s$
 - ☒ D. $(sX(s) - x(0))/s$

Question ID : 4410091524593

Option 1 ID : 4410096021593

Option 2 ID : 4410096021594

Option 3 ID : 4410096021591

Option 4 ID : 4410096021592

Status : Answered

Chosen Option : A

Q.52

The transfer function of a network is given by $H(s) = \frac{(s}{(s +$

- Ans ☒ A. Z=2, P1=4, P2=6
- ☒ B. Z=-2, P1=-4, P2=-6
- ☒ C. Z=-6, P1=-4, P2=-2
- ☒ D. Z=-4, P1=-2, P2=-6

Question ID : 441009266714
Option 1 ID : 4410091036237
Option 2 ID : 4410091036236
Option 3 ID : 4410091036239
Option 4 ID : 4410091036238
Status : Answered
Chosen Option : A

Q.53 Identify the correct statement related to a photodiode.

- Ans ☒ A. The application of light to the junction will result in increased number of minority carriers and a decreased level of reverse current.
- ☒ B. The application of light to the junction will result in increased number of majority carriers and an increased level of reverse current.
- ☒ C. The application of light to the junction will result in increased number of minority carriers and an increased level of reverse current.
- ☒ D. The application of light to the junction will result in increased number of majority carriers and a decreased level of reverse current.

Question ID : 44100929857
Option 1 ID : 441009118885
Option 2 ID : 441009118888
Option 3 ID : 441009118886
Option 4 ID : 441009118887
Status : Answered
Chosen Option : A

Q.54 Choose the INCORRECT statement for the practical diode model.


S1: Equivalent circuit of the practical diode in the forward bias state consist of static resistance only.

S2: Reverse current for the practical diode is zero.

- Ans ☒ A. S1 only
- ☒ B. S2 only
- ☒ C. S1 and S2
- ☒ D. Neither S1 nor S2

Question ID : 4410091506859
Option 1 ID : 4410095951807
Option 2 ID : 4410095951808
Option 3 ID : 4410095951806
Option 4 ID : 4410095951809
Status : Answered
Chosen Option : B

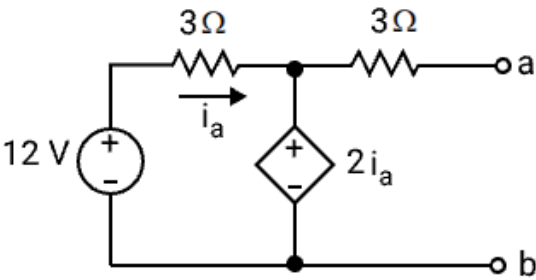Q.55 Determine the Norton equivalent seen between terminals a and b. Select the correct pair of R_N , and i_N .



- Ans ☒ A. $R_N = 3\ \Omega$, $i_N = 1.6\text{ A}$
- ☒ B. $R_N = 4\ \Omega$, $i_N = +3\text{ A}$
- ☒ C. $R_N = 4\ \Omega$, $i_N = -3\text{ A}$
- ☒ D. $R_N = 6\ \Omega$, $i_N = -3\text{ A}$


Question ID : 4410091525800
Option 1 ID : 4410096026353
Option 2 ID : 4410096026351
Option 3 ID : 4410096026350
Option 4 ID : 4410096026352
Status : Answered
Chosen Option : D

Q.56 Choose the correct statement.
S1: The entropy for a fair binary variable with probabilities $P(0) = P(1) = 0.5$ is 1 bit.
S2: If the entropy is computed with natural log (\ln), the unit of entropy is bits.

- Ans ☒ A. S1 and S2
- ☒ B. Only S1
- ☒ C. Neither S1 nor S2
- ☒ D. Only S2

Question ID : 4410091511960
Option 1 ID : 4410095971924
Option 2 ID : 4410095971921
Option 3 ID : 4410095971923
Option 4 ID : 4410095971922
Status : Answered
Chosen Option : A

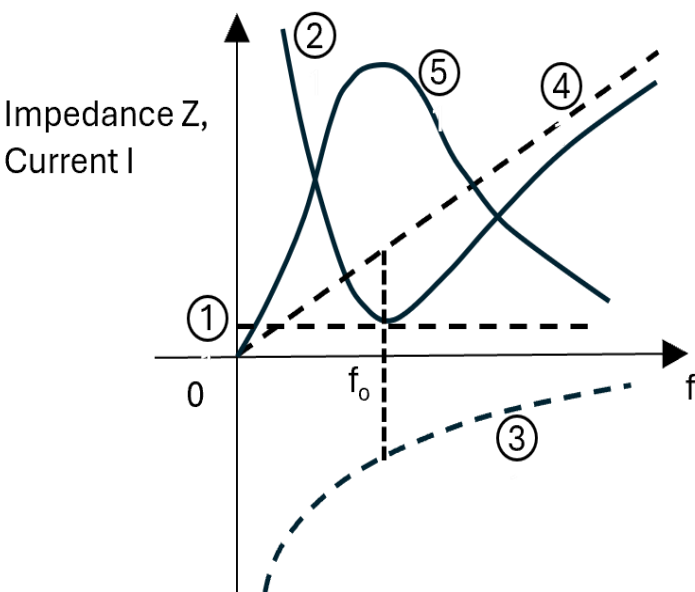Q.57 The figure shows the frequency response of a series R–L–C circuit. Curves are labeled 1 to 5. Which option correctly matches each label to the corresponding quantity?



- Ans
- ☒ A. 1 → R, 2 → |I|, 3 → X_L, 4 → X_C, 5 → |Z|
 - ☒ B. 1 → X_L, 2 → |I|, 3 → X_C, 4 → |Z|, 5 → R
 - ☒ C. 1 → R, 2 → |Z|, 3 → X_C, 4 → X_L, 5 → |I|
 - ☒ D. 1 → |Z|, 2 → R, 3 → X_C, 4 → X_L, 5 → |I|

Question ID : 4410091287469
Option 1 ID : 4410095081665
Option 2 ID : 4410095081664
Option 3 ID : 4410095081663
Option 4 ID : 4410095081666
Status : Answered
Chosen Option : C

Q.58 Determine the DC current gain of the Common collector configuration in NPN BJT, if collector current is 0.98 mA and the base current is 0.02 mA.

- Ans
- ☒ A. 49
 - ☒ B. 50
 - ☒ C. 100
 - ☒ D. 98

Question ID : 4410091506486
Option 1 ID : 4410095950307
Option 2 ID : 4410095950306
Option 3 ID : 4410095950304
Option 4 ID : 4410095950305
Status : Answered
Chosen Option : A

Q.59 Which of the following statements is correct in the context of a semiconductor?

- Ans ☒ A. Concentration of holes in the valence band is independent of the doping concentration in a p-type semiconductor.
- ☒ B. As the temperature increases, thermal energy excites more electrons from the valence band to the conduction band, leaving a higher concentration of holes behind.
- ☒ C. If a pure semiconductor is doped with donor impurities, then the material has a higher hole concentration.
- ☒ D. In a pure semiconductor, the concentration of holes is much greater than the concentration of electrons at thermal equilibrium.

Question ID : 4410091369479
Option 1 ID : 4410095409364
Option 2 ID : 4410095409363
Option 3 ID : 4410095409365
Option 4 ID : 4410095409362
Status : Answered
Chosen Option : B

Q.60 Which of the following facts is true for energy band diagram of n-type semiconductor?

- Ans ☒ A. The doped fermi level overlaps the intrinsic fermi level for rise in doping concentration.
- ☒ B. The doped fermi level moves closer to the conduction band for rise in doping concentration.
- ☒ C. The doped fermi level moves closer to the valence band for rise in doping concentration.
- ☒ D. The fermi level transition is independent of the doping concentration.

Question ID : 4410091369401
Option 1 ID : 4410095409058
Option 2 ID : 4410095409059
Option 3 ID : 4410095409061
Option 4 ID : 4410095409060
Status : Answered
Chosen Option : B

Q.61 Which of the following statements related to the C-V (Capacitance-Voltage) characteristics of a MOS capacitor is correct?

- Ans ☒ A. In accumulation, the capacitance is high and stable, but very much less than the oxide capacitance.
- ☒ B. In accumulation, the capacitance is low and unstable and it much higher than the oxide capacitance.
- ☒ C. In accumulation region, the capacitance is very low but stable and it is equal to the oxide capacitance.
- ☒ D. In accumulation, the capacitance is high and stable, equal to the oxide capacitance.

Question ID : 4410091369208
Option 1 ID : 4410095408287
Option 2 ID : 4410095408289
Option 3 ID : 4410095408286
Option 4 ID : 4410095408288
Status : Answered
Chosen Option : B

Q.62 Which of the following parameters affects the delay time the most in a second-order underdamped system?

- Ans ☒ A. Both natural frequency (ω_n) and damping ratio (ζ)
- ☐ B. Damping ratio ζ only
- ☐ C. Input Amplitude
- ☐ D. Natural frequency ω_n only

Question ID : 441009308830
Option 1 ID : 4410091209055
Option 2 ID : 4410091209053
Option 3 ID : 4410091209054
Option 4 ID : 4410091209052
Status : Answered
Chosen Option : A


Q.63 Select the correct statement(s) for the antilog amplifier.

S1: The antilog amplifier uses the nonlinear behaviour of either diodes or transistors.
S2: The antilog amplifier output is temperature independent.
S3: The antilog amplifier is used in computation like multiplication and division.

- Ans ☐ A. S1, S2 and S3
- ☐ B. Only S1 and S2
- ☐ C. Only S2 and S3
- ☒ D. Only S1 and S3

Question ID : 4410091507070
Option 1 ID : 4410095952717
Option 2 ID : 4410095952715
Option 3 ID : 4410095952716
Option 4 ID : 4410095952714
Status : Answered
Chosen Option : A

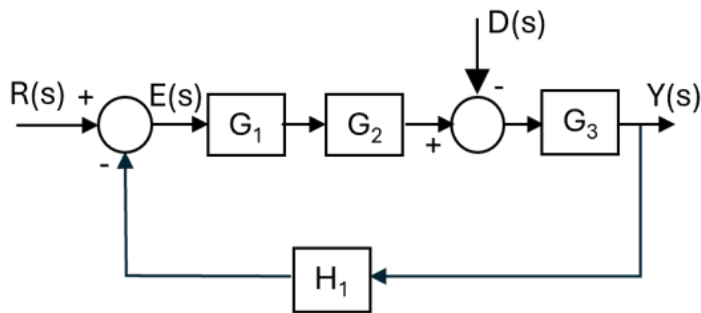Q.64 For the system shown, determine the transfer function $Y(s)/D(s)$. (Take $R(s)=0$.)



- Ans
- ☒ A. $\frac{G_3(s)}{1 + G_1(s)G_2(s)G_3(s)H_1(s)}$
 - ☒ B. $\frac{-G_3(s)}{1 - G_1(s)G_2(s)G_3(s)H_1(s)}$
 - ☒ C. $\frac{-G_3(s)}{1 + G_1(s)G_2(s)G_3(s)H_1(s)}$
 - ☒ D. $\frac{G_3(s)}{1 - G_1(s)G_2(s)G_3(s)H_1(s)}$

Question ID : 4410091454139
Option 1 ID : 4410095744873
Option 2 ID : 4410095744876
Option 3 ID : 4410095744874
Option 4 ID : 4410095744875
Status : Answered
Chosen Option : D

Q.65 A series RC circuit consists of a resistor R and a capacitor C connected in series. A unit-impulse voltage $v_{in}(t) = \delta(t)$ is applied across the circuit. The output is the capacitor voltage $v_c(t)$. The expression correctly representing $v_c(t)$ is _____.

- Ans
- ☒ A. $v_c(t) = e^{-t/RC} u(t)$
 - ☒ B. $v_c(t) = (1/R) e^{-t/RC} u(t)$
 - ☒ C. $v_c(t) = \delta(t) - (1/RC) e^{-t/RC} u(t)$
 - ☒ D. $v_c(t) = (1/RC) e^{-t/RC} u(t)$

Question ID : 4410091454223
Option 1 ID : 4410095745197
Option 2 ID : 4410095745199
Option 3 ID : 4410095745200
Option 4 ID : 4410095745198
Status : Answered
Chosen Option : C

Q.66 Which of the following options is correct in the context of the practical diode model?

- Ans ☒ A. It has fixed voltage drop when conducting.
- ☒ B. It has infinite resistance when forward biased.
- ☒ C. Equivalent circuit of the practical diode in the forward bias state consists of an open circuit only.
- ☒ D. Reverse current for the practical diode is zero.

Question ID : 4410091363848
Option 1 ID : 4410095387318
Option 2 ID : 4410095387320
Option 3 ID : 4410095387321
Option 4 ID : 4410095387319
Status : Answered
Chosen Option : A

Q.67 In a CMOS inverter (NOT gate), what happens to the output when the input voltage is close to the threshold voltage of the NMOS transistor?

- Ans ☒ A. Both NMOS and PMOS transistors may conduct, causing high current dissipation
- ☒ B. Output is guaranteed logic low
- ☒ C. Output becomes undetermined logic level with no current drawn
- ☒ D. Output is guaranteed logic high

Question ID : 4410091521352
Option 1 ID : 4410096008523
Option 2 ID : 4410096008521
Option 3 ID : 4410096008522
Option 4 ID : 4410096008520
Status : Answered
Chosen Option : A

Q.68 Which antenna radiates through an open aperture formed by a flared waveguide?

- Ans ☒ A. Small loop antenna
- ☒ B. Parabolic reflector
- ☒ C. Patch antenna
- ☒ D. Horn antenna

Question ID : 4410091524971
Option 1 ID : 4410096023082
Option 2 ID : 4410096023081
Option 3 ID : 4410096023079
Option 4 ID : 4410096023080
Status : Answered
Chosen Option : C

Q.69 Which of the given statements is correct in the context of the single side band amplitude modulation method or SSB modulation?

S1: Coherent detection demodulation technique is used.

S2: If there is a local oscillator that is 10° out of phase from the required phase, then the output is not distorted.

- Ans ☒ A. S2 only
☒ B. S1 and S2
☒ C. S1 only
☒ D. Neither S1 nor S2

Question ID : 4410091372196

Option 1 ID : 4410095420199

Option 2 ID : 4410095420200

Option 3 ID : 4410095420198

Option 4 ID : 4410095420201

Status : Answered

Chosen Option : A

Q.70 What is the Z- transform $X(z)$ of the signal $x(n) = 3x_1(n) - 2x_2(n)$, where:

$$x_1(n) \xrightarrow{z} X_1(z)$$

$$x_2(n) \xrightarrow{z} X_2(z)$$

- Ans ☒ A. $X(z) = 3X_1(z) - 2X_2(z)$
☒ B. $X(z) = X_1(z) - X_2(z)$
☒ C. $X(z) = x_1(n) + x_2(n)$
☒ D. $X(z) = 3x_1(z) \times x_2(z)$

Question ID : 441009290264

Option 1 ID : 4410091127984

Option 2 ID : 4410091127983

Option 3 ID : 4410091127985

Option 4 ID : 4410091127986

Status : Answered

Chosen Option : A

Q.71 For a good conductor at $f = 10\text{ MHz}$, the attenuation constant is measured as: $\alpha = 5 \times 10^2\text{ Np/m}$. The permeability of the conductor is approximately that of free space ($\mu = \mu_0$). Estimate the skin depth (δ) and the phase velocity (v) of the wave in the conductor.

- Ans
- ☒ A. $\delta = 0.2\text{ mm}$, $v = \pi \times 10^4\text{ m/s}$.
 - ☒ B. $\delta = 2\text{ mm}$, $v = 4\pi \times 10^6\text{ m/s}$.
 - ☒ C. $\delta = 2\text{ mm}$, $v = 4\pi \times 10^4\text{ m/s}$.
 - ☒ D. $\delta = 2\text{ mm}$, $v = 2\pi \times 10^4\text{ m/s}$.

Question ID : 4410091455650
Option 1 ID : 4410095750922
Option 2 ID : 4410095750919
Option 3 ID : 4410095750920
Option 4 ID : 4410095750921
Status : Answered
Chosen Option : B

Q.72 The characteristic equation of a system is given as $a_0s^3 + a_1s^2 + a_2s + a_3 = 0$, where coefficients a_0 , a_1 , a_2 , and a_3 are real and positive numbers. By using the Routh-Hurwitz test, which of the following expressions is a necessary condition for the system to be stable?

- Ans
- ☒ A. $a_1a_3 > a_0a_2$
 - ☒ B. $a_1a_2 > a_0a_3$
 - ☒ C. $a_0a_3 > a_1a_2$
 - ☒ D. $a_0a_1 > a_2a_3$

Question ID : 4410091169063
Option 1 ID : 4410094610731
Option 2 ID : 4410094610729
Option 3 ID : 4410094610728
Option 4 ID : 4410094610730
Status : Answered
Chosen Option : A

Q.73 Which of the following options is correct in the context of a two-way parallel clipper circuit?

- Ans
- ☒ A. The two diodes are connected in parallel but facing the same direction.
 - ☒ B. The two diodes are connected in parallel but in the opposite direction.
 - ☒ C. The two diodes are connected in series but in the opposite direction.
 - ☒ D. The two diodes are connected in series with the load.

Question ID : 4410091363830
Option 1 ID : 4410095387247
Option 2 ID : 4410095387248
Option 3 ID : 4410095387249
Option 4 ID : 4410095387246
Status : Answered
Chosen Option : B

Q.74 Which of the following statements correctly describes the s-domain shifting property?

- Ans ☒ A. Multiplying the signal $x(t)$ by a units in the time domain \leftrightarrow multiplying the signal $X(s)$ by $e-as$.
- ☒ B. Multiplying the signal by $e-at$ in the time domain \leftrightarrow shifting in the s-domain $X(s)$ to $X(s - a)$
- ☒ C. Multiplying the signal by $e-at$ in the time domain \leftrightarrow shifting in the s-domain $X(s)$ to $X(s + 2a)$.
- ☒ D. Multiplying the signal by $t.eat$ in the time domain \leftrightarrow shifting in the s-domain $X(s)$ to $X(s - at)$

Question ID : 4410091385120

Option 1 ID : 4410095471226

Option 2 ID : 4410095471225

Option 3 ID : 4410095471224

Option 4 ID : 4410095471227

Status : Answered

Chosen Option : C

Q.75 A pair of magnetically coupled coils is wound on a nonmagnetic core. The self-inductance of coil 1 is $L_1 = 200$ mH. The mutual inductance is $M = 80$ mH, and the coefficient of coupling is $k = 4/5$. The partial self-permeances are equal, so $L \propto N^2$ with the same proportionality for both coils. Find the self-inductance L_2 of coil 2 and the turns ratio N_1/N_2 .

- Ans ☒ A. $L_2 = 200$ mH, $N_1/N_2 = 2$
- ☒ B. $L_2 = 12.5$ mH, $N_1/N_2 = 2$
- ☒ C. $L_2 = 50$ mH, $N_1/N_2 = 1/2$
- ☒ D. $L_2 = 50$ mH, $N_1/N_2 = 2$

Question ID : 4410091525775

Option 1 ID : 4410096026261

Option 2 ID : 4410096026260

Option 3 ID : 4410096026259

Option 4 ID : 4410096026258

Status : Answered

Chosen Option : D

Q.76 A third-order LTI system has three distinct real poles at $p_1 = -0.8$, $p_2 = -4$ and $p_3 = -15$. A new system $G'(s)$ is formed by adding a zero at $s = -3$ to the original transfer function (the pole locations remain unchanged). Which statement about the unit-step response of $G'(s)$ (compared to the original system $G(s)$) is FALSE?

- Ans ☒ A. $G'(s)$ will generally have a faster rise time than $G(s)$.
- ☒ B. The zero at $s = -3$ will introduce an initial undershoot (inverse response) in the step output of $G'(s)$.
- ☒ C. The dominant pole for both systems remains at $s = -0.8$.
- ☒ D. For a unit-step input, if both systems are adjusted to have unity DC gain, the final value of the response will be the same.

Question ID : 4410091454337
Option 1 ID : 4410095745661
Option 2 ID : 4410095745664
Option 3 ID : 4410095745663
Option 4 ID : 4410095745662
Status : Answered
Chosen Option : D

Q.77 In the CMOS implementation of a NOT gate, which of the following statements is true?

- Ans ☒ A. Both NMOS and PMOS transistors are ON in the steady state.
- ☒ B. When the input is HIGH, NMOS transistor is ON, and PMOS transistor is OFF.
- ☒ C. When the input is HIGH, PMOS transistor is ON, and NMOS transistor is OFF.
- ☒ D. When the input is LOW, NMOS transistor is ON, PMOS transistor is OFF.

Question ID : 4410091521131
Option 1 ID : 4410096007702
Option 2 ID : 4410096007705
Option 3 ID : 4410096007703
Option 4 ID : 4410096007704
Status : Answered
Chosen Option : C

Q.78 A unity negative feedback system has a closed-loop transfer function obtained from the block diagram as:
 $T(s) = C/R = 5/6$.
A student converts the system into a signal-flow graph (SFG) but forgets to include the feedback branch. Using the incomplete SFG, the student computes C/R . From this information, determine the ratio of the incorrect SFG result to the correct block-diagram result.

- Ans ☒ A. 6
- ☒ B. 1/6
- ☒ C. 11/6
- ☒ D. 5/6

Question ID : 4410091524785
Option 1 ID : 4410096022347
Option 2 ID : 4410096022348
Option 3 ID : 4410096022350
Option 4 ID : 4410096022349
Status : Answered
Chosen Option : B

Q.79 When designing a traffic light controller using a Mealy finite state machine, which has three states: S0 (Green), S1 (Yellow), and S2 (Red), the controller utilises a vehicle sensor input X (where 1 indicates a vehicle is present and 0 means no vehicle). Then the output Y = 1 occurs only when _____.

- Ans ☒ A. the machine is in state S1 or S2, and the sensor input X = 1
- ☐ B. the machine is in state S1 and S2, and the sensor input X = 0
- ☐ C. the machine is in state S1 or S2 and the sensor input X = 0
- ☐ D. the machine is in state S1 and the sensor input X = 1

Question ID : 4410091536561
Option 1 ID : 4410096069436
Option 2 ID : 4410096069437
Option 3 ID : 4410096069438
Option 4 ID : 4410096069439
Status : Answered
Chosen Option : B

Q.80 When a control system is represented as a Block Diagram (BD) or a Signal Flow Graph (SFG), both can show feedback and signal paths. Which statement is always true about the relation between these two forms?

- Ans ☐ A. If two Block Diagrams give the same transfer function, their Signal Flow Graphs will also have identical sets of loops and non-touching loop pairs.
- ☒ B. If a Block Diagram has no feedback loops, then its Signal Flow Graph will also have no loops, and $\Delta = 1$ in Mason's formula.
- ☐ C. Moving a signal pickoff point across a block never changes the loop structure, so the SFG is always the same.
- ☐ D. If a Block Diagram contains an instantaneous feedback (called an algebraic loop), then the equivalent Signal Flow Graph must have at least one closed loop, and the system will give a valid transfer function only when $\Delta = 0$.

Question ID : 4410091452223
Option 1 ID : 4410095737303
Option 2 ID : 4410095737300
Option 3 ID : 4410095737302
Option 4 ID : 4410095737301
Status : Answered
Chosen Option : D

Q.81 A common-emitter amplifier using the approximate h-model, has $h_{fe}=200$ and $h_{ie}=2\text{ k}\Omega$. If the input AC voltage is 20 mV, then the base current, collector current and the input resistance are _____, respectively.

- Ans ☐ A. 10 $\mu\text{ A}$, 2m A and 100 K Ω
- ☐ B. 100 $\mu\text{ A}$, 20 m A and 2K Ω
- ☒ C. 10 $\mu\text{ A}$, 2m A and 2K Ω
- ☐ D. 10 m A, 20 $\mu\text{ A}$ and 1K Ω

Question ID : 4410091507089
Option 1 ID : 4410095952793
Option 2 ID : 4410095952791
Option 3 ID : 4410095952790
Option 4 ID : 4410095952792
Status : Answered
Chosen Option : A

Q.82 A circularly polarized plane wave is incident from air ($\epsilon_{r1} = 1$) onto a lossless dielectric medium ($\epsilon_{r2} = 3$). The media are nonmagnetic. The wave is incident at the Brewster angle θ_p . The Brewster angle and the resulting polarization of the reflected wave are _____.

- Ans
- ☒ A. $\theta_p = 30^\circ$, reflected wave remains circularly polarized
 - ☒ B. $\theta_p = 45^\circ$, reflected wave becomes elliptically polarized
 - ☒ C. $\theta_p = 60^\circ$, reflected wave becomes linearly polarized with E perpendicular to the plane of incidence
 - ☒ D. $\theta_p = 60^\circ$, reflected wave becomes linearly polarized with E parallel to the plane of incidence

Question ID : 4410091525089
Option 1 ID : 4410096023550
Option 2 ID : 4410096023551
Option 3 ID : 4410096023553
Option 4 ID : 4410096023552
Status : Answered
Chosen Option : C

Q.83 The transfer function of a system is given below.

$$\frac{5s^2 + 3s + 1}{s^3 + 6s^2 + 11s + 6}$$

Which of the following is the order of this system?

- Ans
- ☒ A. Second order
 - ☒ B. Fourth order
 - ☒ C. First order
 - ☒ D. Third order

Question ID : 4410091169141
Option 1 ID : 4410094611033
Option 2 ID : 4410094611035
Option 3 ID : 4410094611032
Option 4 ID : 4410094611034
Status : Answered
Chosen Option : B

Q.84 A hollow conducting sphere has inner radius a and outer radius b . A point charge $+q$ is fixed at the center of the cavity. The conductor is initially neutral and in electrostatic equilibrium. Consider a concentric closed surface S of radius r with $a < r < b$ (i.e., entirely within the conducting material). The value of $\oint_S \mathbf{E} \cdot d\mathbf{S}$ is _____.

- Ans
- ☒ A. $(2q / \epsilon_0)$
 - ☒ B. $(-q / \epsilon_0)$
 - ☒ C. (q / ϵ_0)
 - ☒ D. 0

Question ID : 4410091455518

Option 1 ID : 4410095750394

Option 2 ID : 4410095750393

Option 3 ID : 4410095750392

Option 4 ID : 4410095750391

Status : Answered

Chosen Option : C

Q.85 A CMOS inverter fabricated in a $0.18 \mu\text{m}$ process for which $V_{DD} = 1.8 \text{ V}$, magnitude of threshold voltage = 0.5 V , $\mu_n = 4 \mu_p$, $\mu_n C_{ox} = 300 \mu\text{A/V}^2$ and Q_N and Q_p have $L_p = 18 \mu\text{m}$ $(W/L)_n = 1.5$, then the value of width W_p is _____.

- Ans
- ☒ A. $4.32 \mu\text{m}$
 - ☒ B. $0.27 \mu\text{m}$
 - ☒ C. $108 \mu\text{m}$
 - ☒ D. $0.54 \mu\text{m}$

Question ID : 4410091380189

Option 1 ID : 4410095451968

Option 2 ID : 4410095451967

Option 3 ID : 4410095451966

Option 4 ID : 4410095451969

Status : Answered

Chosen Option : C

Q.86 Determine the small-signal AC voltage gain of a BJT common-emitter (CE) amplifier with a fully bypassed emitter resistor if the transconductance is 100 mS and the collector resistor and the load resistor are 2 K Ω each. What is the output voltage if the input voltage is $V_{in} = 10\sin(100\pi t)$ mV.

- Ans
- ☒ A. Voltage gain = -100, $V_o = -10\sin(100\pi t)$.
 - ☒ B. Voltage gain = +10, $V_o = \sin(100\pi t)$.
 - ☒ C. Voltage gain = +10, $V_o = 10 \sin(100\pi t)$.
 - ☒ D. Voltage gain = -100, $V_o = -\sin(100\pi t)$.

Question ID : 4410091369202
Option 1 ID : 4410095408264
Option 2 ID : 4410095408262
Option 3 ID : 4410095408265
Option 4 ID : 4410095408263
Status : Answered
Chosen Option : B

Q.87 If analog filter is stable, then which of the following methods guarantees stability of an IIR filter?

- Ans
- ☒ A. Impulse invariance method
 - ☒ B. Fourier series truncation
 - ☒ C. Bilinear transform method
 - ☒ D. Frequency sampling method

Question ID : 4410091409891
Option 1 ID : 4410095568467
Option 2 ID : 4410095568470
Option 3 ID : 4410095568468
Option 4 ID : 4410095568469
Status : Answered
Chosen Option : D

Q.88 Choose the correct statement for a negative clamper circuit.

S1: A clamper circuit is used to add an AC voltage to its input signal.
S2: A negative DC can be added to the input signal in case of a negative clamper circuit.
S3: This circuit uses only diode and resister.

- Ans
- ☒ A. S1 and S3 only
 - ☒ B. S1 and S2 only
 - ☒ C. S2 and S3 only
 - ☒ D. S1, S2 and S2

Question ID : 4410091509995
Option 1 ID : 4410095964661
Option 2 ID : 4410095964660
Option 3 ID : 4410095964662
Option 4 ID : 4410095964663
Status : Answered
Chosen Option : D

Q.89 A rectangular waveguide of internal width $a = 3\text{ cm}$ carries the dominant TE_{10} mode of a signal at unknown frequency. The characteristic wave impedance in the guide is $Z = 240\pi\ \Omega$. Take free-space impedance $Z_0 = 120\pi\ \Omega$ and $c = 3 \times 10^8\text{ m/s}$. Find the operating frequency f .

- Ans ☒ A. $(5/\sqrt{3})\text{ GHz}$
☒ B. $(10/\sqrt{3})\text{ GHz}$
☒ C. $(5\sqrt{3}/2)\text{ GHz}$
☒ D. $(10/3)\text{ GHz}$

Question ID : 4410091456118
Option 1 ID : 4410095752822
Option 2 ID : 4410095752823
Option 3 ID : 4410095752825
Option 4 ID : 4410095752824
Status : Answered
Chosen Option : B

Q.90 A series R–C circuit consists of a resistor R and a capacitor C connected in series. The input is a delayed unit impulse voltage $v_{in}(t) = \delta(t - T)$, $T > 0$. The output is the capacitor voltage $v_C(t)$. Which expression correctly represents $v_C(t)$?

- Ans ☒ A. $v_C(t) = e^{-t/RC} u(t)$
☒ B. $v_C(t) = \delta(t-T) - (1/RC) e^{-(t-T)} / RC u(t-T)$
☒ C. $v_C(t) = (1/RC) e^{-(t-T)} / RC u(t)$
☒ D. $v_C(t) = (1/RC) e^{-(t-T)} / RC u(t-T)$

Question ID : 4410091524943
Option 1 ID : 4410096022971
Option 2 ID : 4410096022974
Option 3 ID : 4410096022972
Option 4 ID : 4410096022973
Status : Answered
Chosen Option : A

Q.91 If frequency modulated signal has message bandwidth of 05 KHz and maximum frequency deviation of 75KHz, the value of modulation index β and bandwidth of the tone FM signal are _____, respectively

- Ans ☒ A. 15 and 160 KHz
☒ B. 7.75 and 160 KHz
☒ C. 7.75 and 80 KHz
☒ D. 15 and 80 MHz

Question ID : 4410091511950
Option 1 ID : 4410095971885
Option 2 ID : 4410095971887
Option 3 ID : 4410095971888
Option 4 ID : 4410095971886
Status : Answered
Chosen Option : C

Q.92 An EM wave of frequency f propagates in a non-magnetic medium ($\mu_r = 1$). The medium parameters are chosen such that $\sigma = \omega\epsilon$ (that is, $\sigma/(\omega\epsilon) = 1$), where $\omega = 2\pi f$ and $\epsilon = \epsilon_0 \epsilon_r$. What is the phase difference between the electric field E and the magnetic field H ? (Assume the usual phasor convention.)

Ans ☒ A. 22.5°

☐ B. 45°

☐ C. 90°

☐ D. 0°

Question ID : 4410091455610

Option 1 ID : 4410095750760

Option 2 ID : 4410095750761


Option 3 ID : 4410095750762

Option 4 ID : 4410095750759

Status : Answered

Chosen Option : B

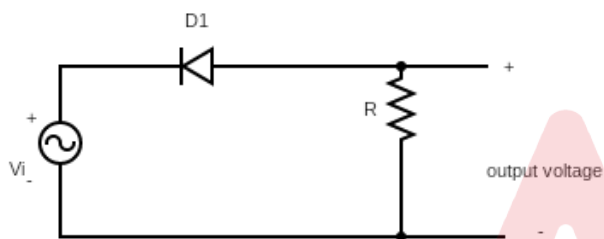Q.93 Study the given circuit carefully and answer the question that follows.



Which of the given statements are correct for the above circuit?

S1: It is a series positive clipper circuit.

S2: For the positive input voltage, output is clipped off.

S3: Output will be negative when the diode is forward biased.

Ans ☐ A. S2 and S3 only

☐ B. S1 and S3 only

☒ C. S1, S2 and S3

☐ D. S1 and S2 only

Question ID : 4410091367456

Option 1 ID : 4410095401272

Option 2 ID : 4410095401270

Option 3 ID : 4410095401269

Option 4 ID : 4410095401271

Status : Answered

Chosen Option : B

Q.94 The transfer function of the discrete-time system $H(z)$ has poles at $z = 0.5$ and $z = 1.5$. Which ROC corresponds to the stable and non-causal system?

- Ans
- ☒ A. $|z| = 1$
 - ☒ B. $|z| > 1.5$
 - ☒ C. $0.5 < |z| < 1.5$
 - ☒ D. $|z| < 0.5$

Question ID : 4410091408666
Option 1 ID : 4410095563628
Option 2 ID : 4410095563626
Option 3 ID : 4410095563627
Option 4 ID : 4410095563625
Status : Answered
Chosen Option : D

Q.95 Five equal resistors, each of resistance R , are connected to form a square, with one diagonal placed between opposite corners. Find the equivalent resistance between two adjacent nodes of the square.

- Ans
- ☒ A. $R/2$
 - ☒ B. $4R/5$
 - ☒ C. $3R/4$
 - ☒ D. $5R/8$

Question ID : 4410091525767
Option 1 ID : 4410096026228
Option 2 ID : 4410096026229
Option 3 ID : 4410096026226
Option 4 ID : 4410096026227
Status : Answered
Chosen Option : A

Q.96 The minimum number of check bits in a single error correcting hamming code if the number of message bits in a block is 27 is _____.

- Ans
- ☒ A. 6
 - ☒ B. 5
 - ☒ C. 8
 - ☒ D. 4

Question ID : 4410091377164
Option 1 ID : 4410095440211
Option 2 ID : 4410095440212
Option 3 ID : 4410095440214
Option 4 ID : 4410095440213
Status : Answered
Chosen Option : D

Q.97 A rectangular pulse $x(t)$ of width T has Fourier transform $X(f) = T \text{ sinc}(f.T)$. The main-lobe bandwidth (null-to-null) is:

- Ans ☒ A. $2/T$
☐ B. T
☐ C. $1/T$
☐ D. $1/(2T)$

Question ID : 4410091408216
Option 1 ID : 4410095561831
Option 2 ID : 4410095561832
Option 3 ID : 4410095561829
Option 4 ID : 4410095561830
Status : Answered
Chosen Option : B

Q.98 A pair of magnetically coupled coils is wound on a nonmagnetic form. The self-inductance of coil 1 is $L_1 = 162 \text{ mH}$, the mutual inductance is $M = 81 \text{ mH}$, and the coefficient of coupling is $k = 0.75$. The physical arrangement is such that the partial self-permeances are equal. Find L_2 and the turns ratio N_1/N_2 .

- Ans ☐ A. $L_2 = 288 \text{ mH}$, $N_1/N_2 = 1/2$
☐ B. $L_2 = 18 \text{ mH}$, $N_1/N_2 = 3/2$
☒ C. $L_2 = 72 \text{ mH}$, $N_1/N_2 = 3/2$
☐ D. $L_2 = 72 \text{ mH}$, $N_1/N_2 = 2/3$

Question ID : 4410091497920
Option 1 ID : 4410095916703
Option 2 ID : 4410095916702
Option 3 ID : 4410095916700
Option 4 ID : 4410095916701
Status : Answered
Chosen Option : A

Q.99 Design a pure parallel RLC resonant circuit having the following parameters:
• $k = 2000 \Omega$ (equivalent parallel resistance)
• $Q = 10$ (quality factor)
• $\omega_0 = 5000 \text{ rad/s}$ (resonant angular frequency)
Determine the values of the inductance L and capacitance C of the circuit.

- Ans ☐ A. $L = 20 \text{ mH}$, $C = 1 \mu\text{F}$
☐ B. $L = 80 \text{ mH}$, $C = 0.5 \mu\text{F}$
☒ C. $L = 40 \text{ mH}$, $C = 1 \mu\text{F}$
☐ D. $L = 10 \text{ mH}$, $C = 4 \mu\text{F}$

Question ID : 4410091498032
Option 1 ID : 4410095917189
Option 2 ID : 4410095917191
Option 3 ID : 4410095917188
Option 4 ID : 4410095917190
Status : Answered
Chosen Option : B

Q.100 Which of the following 8085 instructions uses indirect addressing mode?

- Ans
- ☒ A. LXI H, 2310H
 - ☒ B. MVI A, 32H
 - ☒ C. ADD B
 - ☒ D. MOV A, M

Question ID : 4410091521969

Option 1 ID : 4410096011010

Option 2 ID : 4410096011012

Option 3 ID : 4410096011013

Option 4 ID : 4410096011011

Status : Answered

Chosen Option : A

