

CS/BCA(C)/ODD/SEM-1/1000079/2024-2025/1055



MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL

Paper Code : BCAC101 Digital Electronics

UPID : 1000079

Time Allowed : 3 Hours

Full Marks :70

The Figures in the margin indicate full marks.

Candidate are required to give their answers in their own words as far as practicable

Group-A (Very Short Answer Type Question)

1. Answer any ten of the following :

[1 x 10 = 10]

- $A.A' = ?$
- Full subtractor has _____ number of inputs.
- _____ flip flop is used to store data.
- Mod-10 counter can count upto _____.
- Convert the decimal number 739 to its excess-3 form.
- $AB'C$ is a _____ (minterm/maxterm)
- If A and B are the inputs to a half subtractor then what is the logic expression for Borrow out?
- In a 8X1 MUX, the number of select lines will be _____.
- In a 4 bit RING counter what is the number of states?
- Convert the binary number 1110111 to its equivalent gray code.
- If the number of variables is n then the number of cells in KMap is _____.
- _____ gate is also known as a controlled inverter.

Group-B (Short Answer Type Question)

Answer any three of the following :

[5 x 3 = 15]

- Write a short note on D flip flop. [5]
- Design a 3 bit Asynchronous Down Counter. [5]
- Represent -21.75 in IEEE 754 single precision format. [5]
- State De Morgan's Theorems and proof using truth table. [5]
- Design a 4 bit SIPO register. [5]

Group-C (Long Answer Type Question)

Answer any three of the following :

[15 x 3 = 45]

- Design a 3 bit Asynchronous Up-Down Counter. [6]
 - Design a Decade ripple counter. [6]
 - Explain the method of frequency division in brief. [3]
- Convert the binary number 10110 to its equivalent decimal number. [1]
 - Convert the binary number 10110 to its equivalent octal number. [1+1+1+1+1=5]
 - Convert the binary number 10110 to its equivalent hexadecimal number. [1]
 - Convert the binary number 10110 to its equivalent gray code.
 - Determine 1's complement of the binary number 10110.
 - Write a short note on Parity Generator and Parity Checker.
 - Explain XOR gate and XNOR gate with logic symbol, logic expression, and truth table.
- Find the complement of the Boolean expression: $Y=ABC+ABC'+A'B'C+A'BC$ [3+3+3+6]
 - Prove that $(A+C)(A+D)(B+C)(B+D)=AB+CD$ [1]
 - Simplify the following Boolean expression: $A+A'B'+BC'D'+BC$
 - Obtain minimal POS for the expression: $F(A,B,C,D)=\sum m(3,4,6,7,11,12,13,14,15)$
- Describe full adder with block diagram, truth table, Boolean expression, logic circuit. [5]
 - Draw a half subtractor circuit and describe its operations. [5]
 - Draw a full adder using two half adders. [5]
- Using the k map method simplify the Boolean function to obtain i) minimal SOP ii) minimal POS: $y=\sum m(0,2,3,6,7)+\sum d(8,10,11,15)$ [5+5]
 - Derive the SOP expression from the given truth table where A, B, C are inputs and Y is the output. [5]

Adda247

Test Prime

ALL EXAMS, ONE SUBSCRIPTION



1,00,000+
Mock Tests



**Personalised
Report Card**



**Unlimited
Re-Attempt**



600+
Exam Covered



25,000+ Previous
Year Papers



500%
Refund



ATTEMPT FREE MOCK NOW

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

*** END OF PAPER ***



<https://www.makaut.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से