

HRRL Engineer

Previous Year Paper

(Electrical)

15 Apr, 2025 Shift 1

Adda247

Test Prime

ALL EXAMS, ONE SUBSCRIPTION



80,000+
Mock Tests



**Personalised
Report Card**



**Unlimited
Re-Attempt**



600+
Exam Covered



20,000+ Previous
Year Papers



500%
Refund



ATTEMPT FREE MOCK NOW




HPCL RAJASTHAN REFINERY LIMITED
 Joint Venture between Hindustan Petroleum Corporation Limited (HPCL) and Government of Rajasthan.
Site Office - Village Sajiyali Roonji Kanthwada & Sambhara, Tehsil - Pachpadra, Dist - Balotra, Rajasthan, India - 344032
Reg. Office : Tel Bhavan, Sahkar Marg, Lal Kothi Vistar, Jyoti Nagar, Jaipur, Rajasthan, India 302005
 CIN No. U23201RJ2013GOI043865

Participant ID	
Participant Name	
Test Center Name	
Test Date	15/04/2025
Test Time	9:00 AM - 11:00 AM
Subject	Engineer Electrical

Section : Intellectual Potential Test

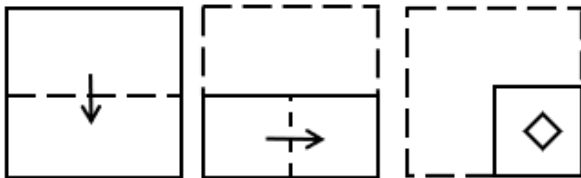Q.1 A paper is folded and cut as shown below. How will it appear when unfolded?




Ans

- ✗ 1.
- ✗ 2.
- ✓ 3.
- ✗ 4.

Question ID : 44100953317
 Option 1 ID : 441009228026
 Option 2 ID : 441009228023
 Option 3 ID : 441009228025
 Option 4 ID : 441009228024
 Status : Answered
 Chosen Option : 3

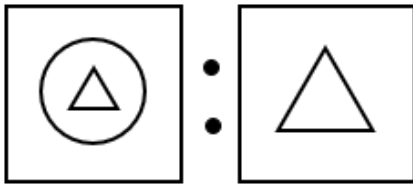Q.2 Figure A is related to figure B following a certain pattern. Select the pair from the options, in which the two figures are related following the same pattern.




(A)

(B)

Ans


✗ 1.

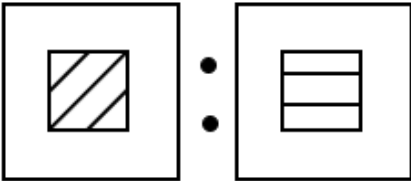

(A)

(B)


✓ 2.

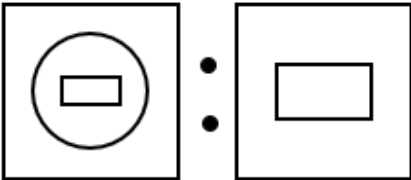

(A)

(B)


✗ 3.

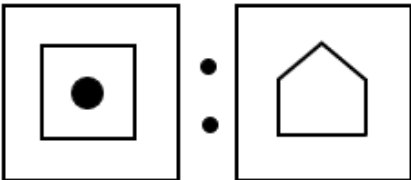

(A)

(B)

✗ 4.

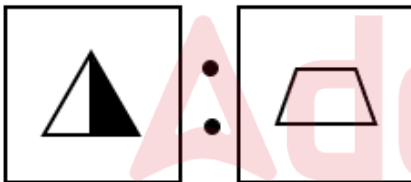

(A)

(B)

Question ID : 44100957997

Option 1 ID : 441009234380

Option 2 ID : 441009234379

Option 3 ID : 441009234378

Option 4 ID : 441009234381

Status : Answered

Chosen Option : 2

Q.3 Read the given statements and conclusions carefully. Assuming that the information given in the statements is true, even if it appears to be at variance with commonly known facts, decide which of the given conclusion(s) logically follow(s) from the statements.

Statements:

All kittens are carrots.

All kittens are trees.

All kittens are plumbers.

Conclusions:

(I): All carrots are plumbers.

(II): Some plumbers are trees.

Ans 1. Neither conclusion (I) nor (II) follows.

2. Only conclusion (I) follows.

3. Both conclusions (I) and (II) follow.

4. Only conclusion (II) follows.

Question ID : 441009108820

Option 1 ID : 441009433097

Option 2 ID : 441009433095

Option 3 ID : 441009433098

Option 4 ID : 441009433096

Status : Answered


Chosen Option : 4

Q.4 Identify the figure from the given options, which when put in place of the question mark (?) will logically complete the series?


		○	○ *	?
	△	△	△	
+	+	+	+	

Ans


✗ 1.

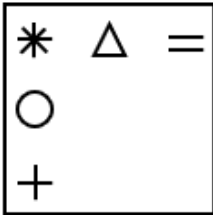


✓ 2.

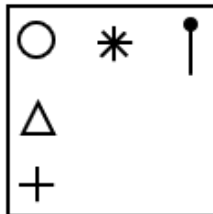

✗ 3.

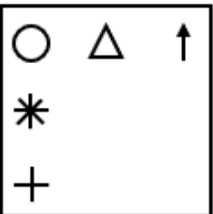

✗ 4.

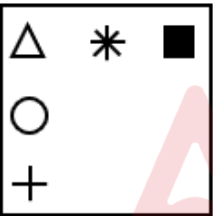

Question ID : 44100957309
 Option 1 ID : 441009234003
 Option 2 ID : 441009234002
 Option 3 ID : 441009234004
 Option 4 ID : 441009234001
 Status : Answered
 Chosen Option : 4

Q.5 MOLECU is related to BDATRJ in a certain way based on the English alphabetical order. In the same way, LIQUID is related to AXFJXS. To which of the given options is MATRIX related, following the same logic?

- Ans 1. BPIHYM
 2. BQJGXM
 3. BPJHXM
 4. BPIGXM

Question ID : 44100964441
 Option 1 ID : 441009256747
 Option 2 ID : 441009256748
 Option 3 ID : 441009256749
 Option 4 ID : 441009256750
 Status : Answered
 Chosen Option : 4

Q.6 यह प्रश्न नीचे दी गई पाँच, तीन-अंकीय संख्याओं पर आधारित है।

(बाएं) 372 938 195 417 693 (दाएं)

(उदाहरण: 697 - पहला अंक = 6, दूसरा अंक = 9 और तीसरा अंक = 7)
 (नोट: सभी संक्रियाएं बाएं से दाएं की जानी हैं।)

यदि सबसे बड़ी संख्या के दूसरे अंक को सबसे छोटी संख्या के तीसरे अंक में जोड़ा जाए, तो परिणाम के रूप में कितना प्राप्त होगा?

- Ans 1. 8
 2. 9
 3. 12
 4. 15

Question ID : 44100919851
 Option 1 ID : 44100979130
 Option 2 ID : 44100979128
 Option 3 ID : 44100979129
 Option 4 ID : 44100979127
 Status : Answered
 Chosen Option : 1

Q.7 प्रबल बिंदु A से शुरू करते हुए दक्षिण की ओर 12 km ड्राइव करता है। फिर वह दाएं मुड़ता है और 32 km ड्राइव करता है। फिर दाएं मुड़ता है और 51 km ड्राइव करता है। फिर दाएं मुड़ता है और 53 km ड्राइव करता है। वह अंतिम बार दाएं मुड़ता है और 39 km ड्राइव करके बिंदु P पर रुक जाता है। बिंदु A पर वापस पहुंचने के लिए उसे कितनी दूरी (न्यूनतम दूरी) और किस दिशा में ड्राइव करना चाहिए? (जब तक निर्दिष्ट न किया जाए, सभी मोड़ 90 डिग्री के मोड़ हैं)

- Ans 1. 24 km पूर्व की ओर
 2. 22 km पश्चिम की ओर
 3. 23 km पूर्व की ओर
 4. 21 km पश्चिम की ओर

Question ID : 44100918840
 Option 1 ID : 44100975135
 Option 2 ID : 44100975133
 Option 3 ID : 44100975134
 Option 4 ID : 44100975132
 Status : Answered
 Chosen Option : 4

Q.8 दिए गए कथनों और निष्कर्षों को ध्यानपूर्वक पढ़ें। यह मानते हुए कि कथनों में दी गई जानकारी सत्य है, भले ही वह सामान्यतः ज्ञात तथ्यों से भिन्न प्रतीत होती हो, तय करें कि दिए गए निष्कर्षों में से कौन-से निष्कर्ष कथनों का तार्किक रूप से अनुसरण करते हैं।

कथन:

सभी गलीचे, मोची हैं।
सभी गलीचे, चूड़ियाँ हैं।
सभी चूड़ियाँ, चटाई हैं।

निष्कर्ष:

(I): सभी गलीचे, चटाई हैं।
(II): कुछ चूड़ियाँ, मोची हैं।

- Ans 1. केवल निष्कर्ष (I) अनुसरण करता है।
 2. केवल निष्कर्ष (II) अनुसरण करता है।
 3. निष्कर्ष (I) और (II) दोनों अनुसरण करते हैं।
 4. न तो निष्कर्ष (I) और न ही निष्कर्ष (II) अनुसरण करता है।

Question ID : 441009108818

Option 1 ID : 441009433090

Option 2 ID : 441009433089

Option 3 ID : 441009433087



Option 4 ID : 441009433088

Status : Answered

Chosen Option : 3

Section : Logical Reasoning and Data interpretation

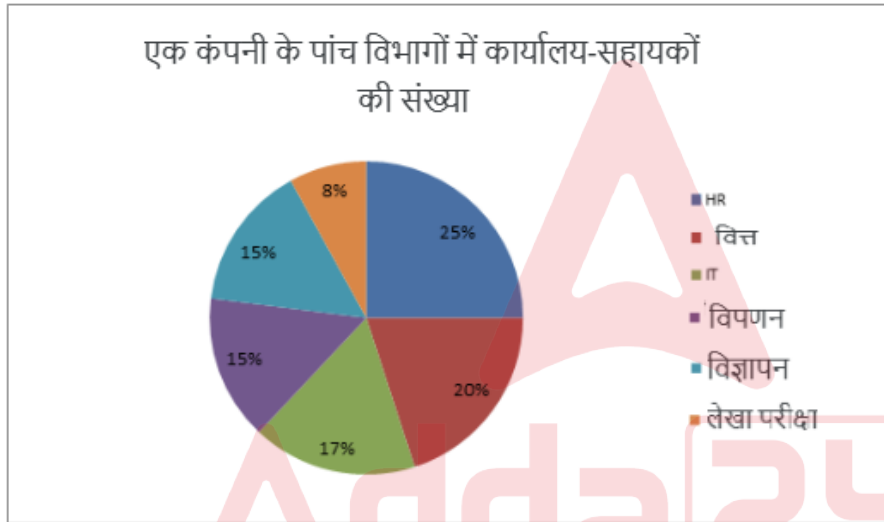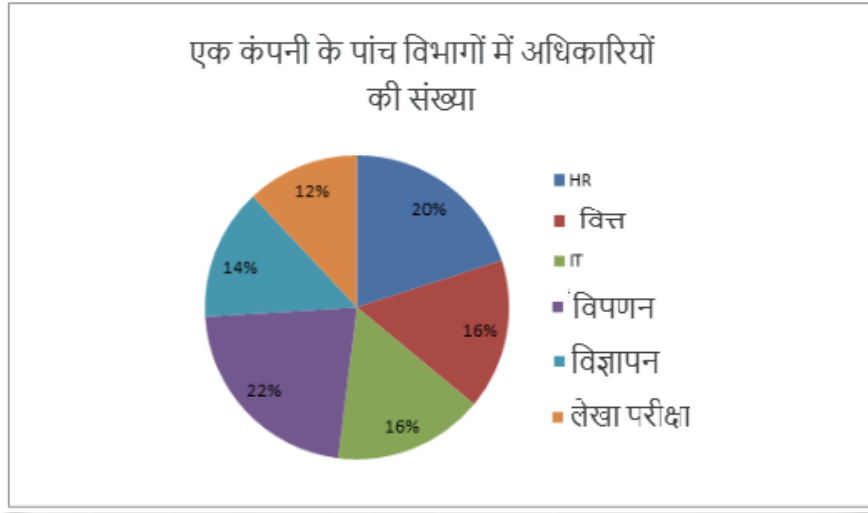Q.1 निम्नांकित पाई चार्ट में एक कंपनी के पाँच विभागों में कार्य करने वाले अधिकारियों और कार्यालय सहायकों की संख्या को दर्शाया गया है। अधिकारियों और कार्यालय सहायकों की कुल संख्या क्रमशः 800 और 1000 है। चार्ट का ध्यानपूर्वक अध्ययन कीजिए और निम्नलिखित प्रश्न का उत्तर दीजिए।



HR, वित्त और विज्ञापन विभागों में अधिकारियों की औसत संख्या, HR, विपणन और IT विभागों में कार्यालय सहायकों की औसत संख्या का कितना प्रतिशत (दशमलव के 2 स्थानों तक पूर्णांकित) है?

- Ans
- 1. 71.67%
 - 2. 68.98%
 - 3. 70.18%
 - 4. 72.56%

Question ID : 44100976413
 Option 1 ID : 441009303892
 Option 2 ID : 441009303889
 Option 3 ID : 441009303890
 Option 4 ID : 441009303891

Status : Answered
 Chosen Option : 3

Q.2 अंग्रेजी वर्णमाला क्रम के आधार पर, निम्नलिखित चार अक्षर-समूह युग्मों में से तीन युग्म एक निश्चित तरीके से समान हैं और इस प्रकार एक ग्रुप बनाते हैं। वह कौन-सा अक्षर-समूह युग्म है, जो उस ग्रुप समूह से संबंधित नहीं है?

(नोट: असंगत अक्षर-समूह युग्म व्यंजनों/स्वरों की संख्या या उनकी स्थिति पर आधारित नहीं है।)

- Ans
- 1. LE : ZS
 - 2. VO : JC
 - 3. EY : UO
 - 4. GZ : UN

Question ID : 44100963050
 Option 1 ID : 441009251236
 Option 2 ID : 441009251237
 Option 3 ID : 441009251238
 Option 4 ID : 441009251235
 Status : Answered
 Chosen Option : 3

Q.3 निम्नलिखित तालिका वर्ष 2010 से 2013 के दौरान एक शहर में स्नातक पुरुषों और महिलाओं की कुल संख्या तथा स्नातकोत्तर पुरुषों और महिलाओं की कुल संख्या दर्शाती है। तालिका का अध्ययन कीजिए और दिए गए प्रश्न का उत्तर दीजिए।

वर्ष	2010	2011	2012	2013
स्नातक पुरुष	1200	1400	1500	1600
स्नातक महिलाएँ	800	900	1000	1200
स्नातकोत्तर पुरुष	1000	1200	1250	1300
स्नातकोत्तर महिलाएँ	600	750	800	900


सभी वर्षों में, स्नातकोत्तर महिलाओं की कुल संख्या, स्नातक पुरुषों की कुल संख्या की कितनी प्रतिशत (दशमलव के 2 स्थानों तक पूर्णांकित) है?

- Ans
- 1. 50.62%
 - 2. 53.51%
 - 3. 52.50%
 - 4. 54.61%

Question ID : 44100968281
 Option 1 ID : 441009274277
 Option 2 ID : 441009274279
 Option 3 ID : 441009274278
 Option 4 ID : 441009274280
 Status : Answered
 Chosen Option : 2

Q.4 निम्नांकित पाई चार्ट में, विभिन्न श्रेणियों (मकान किराया, किराना, शिक्षा, स्वास्थ्य, दान और बचत) एक परिवार का मासिक व्यय दर्शाया गया है। परिवार की कुल आय ₹20,000 है। चार्ट का अध्ययन कीजिए और दिए गए प्रश्न का उत्तर दीजिए।

परिवार का मासिक व्यय

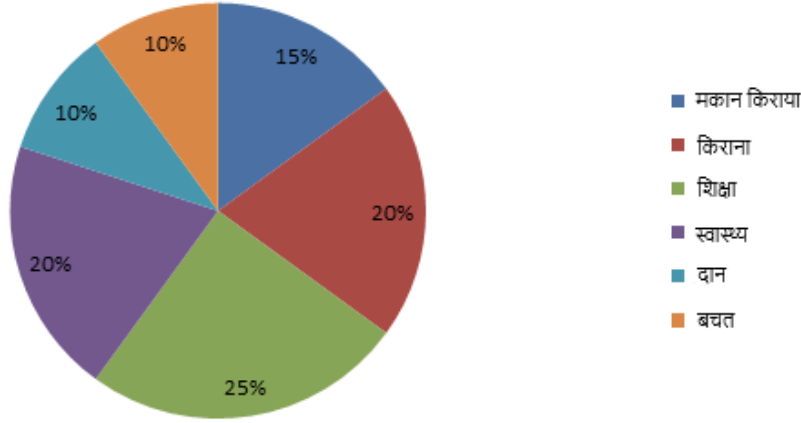

मकान किराया, शिक्षा और स्वास्थ्य पर किया गया कुल व्यय कितना है?

- Ans 1. ₹12,000
 2. ₹14,000
 3. ₹16,000
 4. ₹10,000


Question ID : 44100968929
 Option 1 ID : 441009283533
 Option 2 ID : 441009283531
 Option 3 ID : 441009283532
 Option 4 ID : 441009283534
 Status : Answered
 Chosen Option : 1

Q.5 सात बॉक्स M, N, O, P, S, T और U एक के ऊपर एक रखे गए हैं, लेकिन जरूरी नहीं कि इसी क्रम में रखे गए हों। केवल P को M के ऊपर रखा गया है। M और U के बीच केवल दो बॉक्स रखे गए हैं। केवल N को S के नीचे रखा गया है। O को U के ठीक ऊपर नहीं रखा गया है। T और N के बीच कितने बॉक्स रखे गए हैं?

- Ans 1. दो
 2. तीन
 3. एक
 4. चार

Question ID : 44100918762
 Option 1 ID : 44100974813
 Option 2 ID : 44100974814
 Option 3 ID : 44100974812
 Option 4 ID : 44100974815
 Status : Answered
 Chosen Option : 2

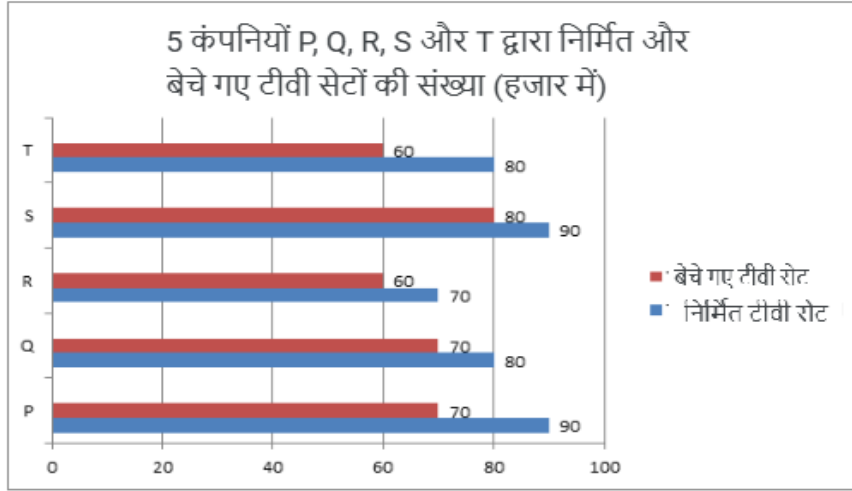Q.6 निम्नलिखित बार आलेख 5 अलग-अलग कंपनियों P, Q, R, S और T द्वारा निर्मित और बेचे गए टेलीविजन सेटों की संख्या (हजार में) दर्शाता है। आलेख का अध्ययन कीजिए और नीचे दिए प्रश्न का उत्तर दीजिए।



कंपनियों Q और S द्वारा बेचे गए टेलीविजन सेटों की औसत संख्या, कंपनियों P, R और T द्वारा निर्मित टेलीविजन सेटों की औसत संख्या की कितनी प्रतिशत है?

- Ans
- 1. 94.64%
 - 2. 92.68%
 - 3. 90.45%
 - 4. 93.75%

Question ID : 44100968921
 Option 1 ID : 441009276168
 Option 2 ID : 441009276171
 Option 3 ID : 441009276169
 Option 4 ID : 441009276170
 Status : Answered

Chosen Option : 4

Q.7 दी गई श्रृंखला को तार्किक रूप से पूर्ण बनाने के लिए, निम्नलिखित में से कौन-सा अक्षर-संख्या समूह प्रश्न-चिह्न (?) के स्थान पर आएगा?

JKG 47 HIE 57 FGC 67 DEA 77 ?

- Ans
- 1. BDX 87
 - 2. BCY 87
 - 3. BGM 86
 - 4. BBX 86

Question ID : 44100923059
 Option 1 ID : 44100991971
 Option 2 ID : 44100991970
 Option 3 ID : 44100991973
 Option 4 ID : 44100991972
 Status : Answered

Chosen Option : 2

Q.8 किसी निश्चित कूट भाषा में,

'A @ B' का अर्थ है कि 'A, B का पुत्र है',
'A - B' का अर्थ है कि 'A, B का भाई है',
'A x B' का अर्थ है कि 'A, B की पत्नी है' और
'A ÷ B' का अर्थ है कि 'A, B का पिता है'।

यदि 'T @ Y x E ÷ W - R' है, तो T का R से क्या संबंध है?

- Ans
- 1. पुत्र
 - 2. पति
 - 3. पिता
 - 4. भाई

Question ID : 44100918799

Option 1 ID : 44100974962

Option 2 ID : 44100974963

Option 3 ID : 44100974960

Option 4 ID : 44100974961

Status : Answered

Chosen Option : 4

Section : Quantitative Aptitude

Q.1 40 आदमी किसी कार्य को 20 दिन में पूरा कर सकते हैं। उन्होंने साथ मिलकर कार्य करना शुरू किया। 10 दिन बाद, 10 और आदमी उनके साथ जुड़ गए। अब उन्हें शेष कार्य पूरा करने में कितने दिन लगेंगे?

- Ans
- 1. 4
 - 2. 10
 - 3. 6
 - 4. 8

Question ID : 44100967284

Option 1 ID : 441009267886

Option 2 ID : 441009267887

Option 3 ID : 441009267888

Option 4 ID : 441009267889

Status : Answered

Chosen Option : 4

Q.2 एक रेलगाड़ी 40 मिनट में 60 km की दूरी तय करती है। एक हवाई जहाज़ की चाल, रेलगाड़ी की चाल से दोगुनी है। हवाई जहाज़ द्वारा 20 मिनट में कितनी दूरी (km में) तय की जाती है?

- Ans
- 1. 45
 - 2. 60
 - 3. 55
 - 4. 50

Question ID : 44100963582

Option 1 ID : 441009253345

Option 2 ID : 441009253344

Option 3 ID : 441009253343

Option 4 ID : 441009253346

Status : Answered

Chosen Option : 2

Q.3 Simplify the following expression.

$$\sqrt{\frac{0.1250 \times 0.040 \times 0.008}{0.002 \times 0.0005 \times 0.025}}$$

Ans 1. 40

2. 20

3. 30

4. 50

Question ID : 44100963533

Option 1 ID : 441009253149

Option 2 ID : 441009253148

Option 3 ID : 441009253147

Option 4 ID : 441009253150

Status : Answered

Chosen Option : 1

Q.4 दो व्यक्तियों A और B की कुल आय बराबर है। हालाँकि, A को उसके मूल वेतन का 60% भत्ते के रूप में प्राप्त होता है और B को उसके मूल वेतन का 50% भत्ते के रूप में प्राप्त होता है। A और B के मूल वेतनों का अनुपात ज्ञात कीजिए।

Ans 1. 16 : 13

2. 15 : 16

3. 13 : 15

4. 14 : 15

Question ID : 44100962804

Option 1 ID : 441009250318

Option 2 ID : 441009250317

Option 3 ID : 441009250316

Option 4 ID : 441009250315

Status : Answered

Chosen Option : 2

Q.5 तेल के मूल्य में 40% की वृद्धि हुई है। यदि कुल व्यय अपरिवर्तित रहता है, तो खपत में कमी और मूल खपत का अनुपात ज्ञात कीजिए।

Ans 1. 2 : 5

2. 3 : 7

3. 2 : 7

4. 1 : 5

Question ID : 44100962795

Option 1 ID : 441009250239

Option 2 ID : 441009250242

Option 3 ID : 441009250241

Option 4 ID : 441009250240

Status : Answered

Chosen Option : 3

Q.6 न्यूनतम कितने वर्षों में, ₹5,000 की धनराशि पर $6\frac{1}{4}\%$ वार्षिक ब्याज दर से प्राप्त साधारण ब्याज, पूर्ण संख्या में रुपयों में प्राप्त होगा?

- Ans 1. 3
 2. 2
 3. 4
 4. 5

Question ID : 44100962833
 Option 1 ID : 441009250381
 Option 2 ID : 441009250379
 Option 3 ID : 441009250380
 Option 4 ID : 441009250382
 Status : Answered
 Chosen Option : 2

Section : English Language

Q.1 Select the most appropriate adjective to fill in the blank.

The mountaineer felt very _____ after climbing the steep mountain trail and sat down to rest.

- Ans 1. hesitant
 2. cognisant
 3. jubilant
 4. lethargic

Question ID : 44100947720
 Option 1 ID : 441009189974
 Option 2 ID : 441009189973
 Option 3 ID : 441009189971
 Option 4 ID : 441009189972
 Status : Answered
 Chosen Option : 4

Q.2 Select the option that can be used as a one-word substitute for the given group of words.

A person who helps the needy

- Ans 1. Alchemist
 2. Samaritan
 3. Misogynist
 4. Optimistic

Question ID : 44100947754
 Option 1 ID : 441009190106
 Option 2 ID : 441009190104
 Option 3 ID : 441009190103
 Option 4 ID : 441009190105
 Status : Answered
 Chosen Option : 2

Q.3 Sentences of a paragraph are given below. While the first and the last sentences (S1 and S6) are in the correct order, the sentences in between are jumbled up. Arrange the sentences in the correct order to form a meaningful and coherent paragraph.

S1. Television has become the most popular source of entertainment these days.

P. A study of the graph showing time spent on watching TV and on reading amply supports my contention.

Q. Young children are fascinated by it.

R. Twenty years ago, a kid would spend 9-10 hours daily on reading.

S. They are quite familiar with TV serials, their stars and the intricacies of their respective plots.

S6. The number of hours devoted to reading have steadily declined and reached the pathetic figure of an hour a day.

Ans 1. RPSQ

2. RSPQ

3. QSPR

4. QPSR

Question ID : 44100947735

Option 1 ID : 441009190030

Option 2 ID : 441009190029

Option 3 ID : 441009190027

Option 4 ID : 441009190028

Status : Answered

Chosen Option : 3

Q.4 Select the most appropriate ANTONYM of the underlined word.

He was labelled a philistine for his open disdain of modern art.

Ans 1. Dynamic

2. Intellectual

3. Plutocrat

4. Libertine

Question ID : 44100948506

Option 1 ID : 441009193332

Option 2 ID : 441009193333

Option 3 ID : 441009193335

Option 4 ID : 441009193334

Status : Answered

Chosen Option : 4

Q.5 Select the most appropriate meaning of the given proverb.

Don't put all your eggs in one basket.

- Ans
- 1. Eggs are fragile and should be handled with care.
 - 2. One should refrain from gratuitous spoilage.
 - 3. Baskets are meant to hold many items.
 - 4. One should not concentrate all efforts and resources in one area as one could lose everything.

Question ID : 44100948511

Option 1 ID : 441009193362

Option 2 ID : 441009193363

Option 3 ID : 441009193361

Option 4 ID : 441009193360

Status : Answered

Chosen Option : 4

Comprehension:

Read the given passage and answers the questions that follow.

There is, of course, no question of belief without evidence. We must beware of confusion between the way in which a Christian first assents to certain propositions and the way in which he afterwards adheres to them. These must be carefully distinguished. Of the second it is true, in a sense, to say that Christians do recommend a certain discounting of apparent contrary evidence. But so far as I know it is not expected that a man should assent to these propositions in the first place without evidence or in the teeth of the evidence. At any rate, if anyone expects that, I certainly do not. And in fact, the man who accepts Christianity always thinks he had good evidence; whether, like Dante, physical or metaphysical arguments, or historical evidence, or the evidence of religious experience, or authority, or all these together. For, of course, authority, however we may value it in this or that particular instance, is a kind of evidence. All of our historical beliefs, most of our geographical beliefs, many of our beliefs about matters that concern us in daily life, are accepted on the authority of other human beings, whether we are Christians, Atheists, Scientists or Men-in-the-Street.

SubQuestion No : 6

Q.6 What type(s) of evidence does the passage suggest might lead a person to accept Christianity?

- Ans
- 1. Physical, metaphysical, historical, experiential, or authoritative evidence or a combination thereof
 - 2. Primarily emotional responses, dismissing logical or historical arguments
 - 3. Only direct, personal religious experiences, excluding any other form of reasoning
 - 4. Solely reliance on philosophical arguments, disregarding any physical proof

Question ID : 44100947942

Option 1 ID : 441009190843

Option 2 ID : 441009190842

Option 3 ID : 441009190841

Option 4 ID : 441009190844

Status : Answered

Chosen Option : 1

Comprehension:

Read the given passage and answers the questions that follow.

There is, of course, no question of belief without evidence. We must beware of confusion between the way in which a Christian first assents to certain propositions and the way in which he afterwards adheres to them. These must be carefully distinguished. Of the second it is true, in a sense, to say that Christians do recommend a certain discounting of apparent contrary evidence. But so far as I know it is not expected that a man should assent to these propositions in the first place without evidence or in the teeth of the evidence. At any rate, if anyone expects that, I certainly do not. And in fact, the man who accepts Christianity always thinks he had good evidence; whether, like Dante, physical or metaphysical arguments, or historical evidence, or the evidence of religious experience, or authority, or all these together. For, of course, authority, however we may value it in this or that particular instance, is a kind of evidence. All of our historical beliefs, most of our geographical beliefs, many of our beliefs about matters that concern us in daily life, are accepted on the authority of other human beings, whether we are Christians, Atheists, Scientists or Men-in-the-Street.

SubQuestion No : 7

Q.7 What is the most suitable title for the given passage?

- Ans
- 1. The Dangers of Blind Faith in Modern Science
 - 2. The Inherent Contradictions within an Atheistic Worldview
 - 3. The Role of Evidence and Authority in Christian Belief
 - 4. The Superiority of Religious Experience over Historical Facts

Question ID : 44100947940

Option 1 ID : 441009190833

Option 2 ID : 441009190836

Option 3 ID : 441009190834

Option 4 ID : 441009190835

Status : Answered

Chosen Option : 3

Comprehension:

Read the given passage and answers the questions that follow.

There is, of course, no question of belief without evidence. We must beware of confusion between the way in which a Christian first assents to certain propositions and the way in which he afterwards adheres to them. These must be carefully distinguished. Of the second it is true, in a sense, to say that Christians do recommend a certain discounting of apparent contrary evidence. But so far as I know it is not expected that a man should assent to these propositions in the first place without evidence or in the teeth of the evidence. At any rate, if anyone expects that, I certainly do not. And in fact, the man who accepts Christianity always thinks he had good evidence; whether, like Dante, physical or metaphysical arguments, or historical evidence, or the evidence of religious experience, or authority, or all these together. For, of course, authority, however we may value it in this or that particular instance, is a kind of evidence. All of our historical beliefs, most of our geographical beliefs, many of our beliefs about matters that concern us in daily life, are accepted on the authority of other human beings, whether we are Christians, Atheists, Scientists or Men-in-the-Street.

SubQuestion No : 8

Q.8 What is the tone of the given passage?

- Ans
- 1. Humorous and satirical
 - 2. Emotional and passionate
 - 3. Analytical and argumentative
 - 4. Condescending and dismissive

Question ID : 44100947941

Option 1 ID : 441009190839

Option 2 ID : 441009190838

Option 3 ID : 441009190840

Option 4 ID : 441009190837

Status : Answered

Chosen Option : 3

Section : Technical Knowledge

Q.1 For a long transmission line, the ABCD parameters are used to characterise its performance. Which of the following describes the relationship between the voltage at the sending end (V_s) and the voltage at the receiving end (V_r) for a transmission line?

- Ans
- 1. $V_s = AV_r + BI_r$
 - 2. $V_s = AV_r + BI_s$
 - 3. $V_r = AV_s + BI_s$
 - 4. $V_r = AV_s + BI_r$

Question ID : 44100949605

Option 1 ID : 441009197689

Option 2 ID : 441009197691

Option 3 ID : 441009197690

Option 4 ID : 441009197692

Status : Answered

Chosen Option : 1

Q.2 The total flux Φ leaving a sphere of radius r , due to a point charge q at the centre is given by:

- Ans 1. $\Phi = q$
2. $\Phi = \frac{q}{4\pi\epsilon_0 r^2}$
3. $\Phi = 4\pi\epsilon_0 q$
4. $\Phi = \frac{q}{\epsilon_0}$

Question ID : 44100989583

Option 1 ID : 441009356512

Option 2 ID : 441009356511

Option 3 ID : 441009356514

Option 4 ID : 441009356513

Status : Answered

Chosen Option : 1

Q.3 In the context of an infinite busbar, which parameter remains constant regardless of the connected alternator's output?

- Ans 1. Reactive power
2. Frequency
3. Current
4. Power factor

Question ID : 44100996241

Option 1 ID : 441009383011

Option 2 ID : 441009383009

Option 3 ID : 441009383008

Option 4 ID : 441009383010

Status : Answered

Chosen Option : 2

Q.4 In Practical Dual converter, circulating current is limited by inserting a/an _____ between two converters.

- Ans 1. inductor
2. fuse
3. capacitor
4. resistor

Question ID : 441009147778

Option 1 ID : 441009587021

Option 2 ID : 441009587024

Option 3 ID : 441009587022

Option 4 ID : 441009587023

Status : Answered

Chosen Option : 1

Q.5 What is the form factor of a sine wave in a full-wave rectifier voltmeter?

- Ans 1. 1.11
 2. 2
 3. 1.57
 4. 0.707

Question ID : 441009120146
Option 1 ID : 441009477643
Option 2 ID : 441009477645
Option 3 ID : 441009477644
Option 4 ID : 441009477646
Status : Answered
Chosen Option : 1

Q.6 Reproducibility in measurements refers to:

- Ans 1. the smallest change in input that an instrument can detect
 2. the ability of an instrument to give an accurate reading
 3. the ability to obtain the same result when the same person repeats a measurement
 4. the ability to obtain consistent results under different conditions

Question ID : 441009116908
Option 1 ID : 441009464761
Option 2 ID : 441009464762
Option 3 ID : 441009464760
Option 4 ID : 441009464759
Status : Answered
Chosen Option : 4

Q.7 For a short-length transmission line, the voltage regulation is primarily influenced by:

- Ans 1. the series reactance and the shunt capacitance
 2. only the series reactance of the line
 3. the series resistance and the line's inductive reactance
 4. the series resistance and the load power factor

Question ID : 44100949657
Option 1 ID : 441009197894
Option 2 ID : 441009197896
Option 3 ID : 441009197895
Option 4 ID : 441009197893
Status : Answered
Chosen Option : 3

Q.8 How does an increase in temperature affect the resistance of the voltage coil?

- Ans
- 1. No effect on resistance
 - 2. Increases resistance
 - 3. Decreases resistance
 - 4. Increases current flow

Question ID : 441009120311
Option 1 ID : 441009478288
Option 2 ID : 441009478286
Option 3 ID : 441009478287
Option 4 ID : 441009478289
Status : Answered
Chosen Option : 2

Q.9 Delay time in IGBT is time for _____.

- Ans
- 1. collector emitter voltage, V_{CE} to fall from V_{CE} to $0.9 V_{CE}$
 - 2. collector current, I_C to rise from $0.9 I_C$ to final value I_C
 - 3. collector current, I_C to rise from $0.1 I_C$ to $0.9 I_C$
 - 4. collector emitter voltage, V_{CE} to fall from $0.9 V_{CE}$ to $0.1 V_{CE}$

Question ID : 441009150870
Option 1 ID : 441009598720
Option 2 ID : 441009598723
Option 3 ID : 441009598722
Option 4 ID : 441009598721
Status : Answered
Chosen Option : 1

Q.10 In a step-down autotransformer with turns ratio of 10 : 5, the inductively transferred power is:

- Ans
- 1. equal to the total power
 - 2. greater than the total power
 - 3. half of the total power
 - 4. independent of the load

Question ID : 441009117083
Option 1 ID : 441009465462
Option 2 ID : 441009465464
Option 3 ID : 441009465463
Option 4 ID : 441009465465
Status : Answered
Chosen Option : 3

Q.11 The critical clearing time depends on which of the following factors in a power system?

- Ans 1. The type of fault and the location of the fault
2. The fault impedance and line resistance
3. The total system load and generation capacity
4. The voltage level at the fault location

Question ID : 44100949039
Option 1 ID : 441009195452
Option 2 ID : 441009195454
Option 3 ID : 441009195453
Option 4 ID : 441009195455
Status : Answered
Chosen Option : 3

Q.12 For a transmission line with an insulator string, if the string efficiency is low, which of the following can be a potential consequence?

- Ans 1. Increased voltage across the first insulator unit, potentially leading to insulation breakdown
2. Increased losses in the transmission line
3. Lower sag in the transmission line
4. Higher mechanical strength of the transmission line

Question ID : 44100949592
Option 1 ID : 441009197642
Option 2 ID : 441009197641
Option 3 ID : 441009197644
Option 4 ID : 441009197643
Status : Answered
Chosen Option : 2

Q.13 In a potential transformer (PT), where is the primary winding connected?

- Ans 1. Load
2. High-voltage circuit
3. Low-voltage circuit
4. Secondary winding

Question ID : 441009120215
Option 1 ID : 441009477911
Option 2 ID : 441009477912
Option 3 ID : 441009477913
Option 4 ID : 441009477914
Status : Answered
Chosen Option : 2

Q.14 Which of the following is a type of power diode?

- Ans 1. Bidirectional thyristor diode
 2. TRIAC
 3. Fast recovery diode
 4. Zener diode

Question ID : 441009150998

Option 1 ID : 441009599227

Option 2 ID : 441009599228

Option 3 ID : 441009599226

Option 4 ID : 441009599225

Status : Answered

Chosen Option : 3

Q.15 The electric field intensity E at a point due to a continuous volume charge density ρ_v is given by:

- Ans 1. $E = \frac{1}{4\pi\epsilon_0} \int \frac{\rho_v dV}{r} \hat{r}$
 2. $E = \frac{\rho_v}{\epsilon_0}$
 3. $E = \frac{1}{4\pi\epsilon_0} \int \rho_v dV$
 4. $E = \frac{1}{4\pi\epsilon_0} \int \frac{\rho_v dV}{r^2} \hat{r}$

Question ID : 44100989760

Option 1 ID : 441009357202

Option 2 ID : 441009357204

Option 3 ID : 441009357203

Option 4 ID : 441009357201

Status : Answered

Chosen Option : 4

Q.16 A step-up chopper has input voltage of 220 V and output voltage of 660 V. If non-conducting time of thyristor is 100 μ s, calculate pulse width of output voltage.

- Ans 1. 100 μ s
 2. 400 μ s
 3. 200 μ s
 4. 300 μ s

Question ID : 441009150825

Option 1 ID : 441009598540

Option 2 ID : 441009598543

Option 3 ID : 441009598541

Option 4 ID : 441009598542

Status : Answered

Chosen Option : 1

Q.17 At what load angle (δ) is maximum power developed in a synchronous motor?

- Ans 1. 0°
 2. 15°
 3. 90°
 4. 45°

Question ID : 441009100040
Option 1 ID : 441009398224
Option 2 ID : 441009398225
Option 3 ID : 441009398227
Option 4 ID : 441009398226
Status : Answered
Chosen Option : 3

Q.18 In a DC machine, the cross-magnetising effect of armature reaction is caused by:

- Ans 1. eddy currents in the armature
 2. armature MMF acting perpendicular to the main field
 3. hysteresis losses
 4. armature MMF acting parallel to the main field

Question ID : 44100989455
Option 1 ID : 441009356233
Option 2 ID : 441009356231
Option 3 ID : 441009356234
Option 4 ID : 441009356232
Status : Answered
Chosen Option : 2

Q.19 A series RLC circuit is in resonance when:

- Ans 1. $X_L > X_C$
 2. $X_C > X_L$
 3. $X_L = X_C$
 4. $R = X_L - X_C$

Question ID : 441009157433
Option 1 ID : 441009624900
Option 2 ID : 441009624901
Option 3 ID : 441009624899
Option 4 ID : 441009624902
Status : Answered
Chosen Option : 3

Q.20 The inductive reactance (X_L) of an inductor depends on:

- Ans
- 1. current and inductance
 - 2. resistance and capacitance
 - 3. voltage and resistance
 - 4. frequency and inductance

Question ID : 441009157409
 Option 1 ID : 441009624804
 Option 2 ID : 441009624806
 Option 3 ID : 441009624803
 Option 4 ID : 441009624805
 Status : Answered
 Chosen Option : 4

Q.21 The distortion factor of a two-pulse converter is:

- Ans
- 1. measure of harmonic content in output frequency
 - 2. measure of harmonic content in output current
 - 3. measure of harmonic content in output voltage
 - 4. measure of harmonic content in input current

Question ID : 441009148635
 Option 1 ID : 441009590365
 Option 2 ID : 441009590363
 Option 3 ID : 441009590362
 Option 4 ID : 441009590364
 Status : Answered
 Chosen Option : 2

Q.22 Gauss's law in differential form is given by:

- Ans
- 1. $\nabla \cdot \mathbf{E} = \rho$
 - 2. $\nabla \times \mathbf{E} = \frac{\rho}{\epsilon_0}$
 - 3. $\nabla \cdot \mathbf{E} = \frac{\rho}{\epsilon_0}$
 - 4. $\nabla \times \mathbf{E} = 0$

Question ID : 44100989555
 Option 1 ID : 441009356401
 Option 2 ID : 441009356400
 Option 3 ID : 441009356399
 Option 4 ID : 441009356402
 Status : Answered
 Chosen Option : 3

Q.23 During an unsymmetrical fault, such as a line-to-line fault, the transmission line typically experiences:

- Ans
- 1. a balanced fault current in all phases
 - 2. a complete voltage drop in the faulted phases only
 - 3. no change in the line's impedance
 - 4. a current unbalance between the faulted phases and the unaffected phase

Question ID : 44100948857

Option 1 ID : 441009194736

Option 2 ID : 441009194739

Option 3 ID : 441009194738

Option 4 ID : 441009194737

Status : Answered

Chosen Option : 4

Q.24 Which of the following circuit elements can store energy and return it to the circuit?

- Ans
- 1. Capacitor and inductor only
 - 2. Resistor only
 - 3. Capacitor only
 - 4. Inductor only

Question ID : 441009159369

Option 1 ID : 441009632330

Option 2 ID : 441009632327

Option 3 ID : 441009632328

Option 4 ID : 441009632329

Status : Answered

Chosen Option : 1

Q.25 Which of the following statements about load sharing in paralleled transformers is true?

- Ans
- 1. Load sharing is independent of impedance.
 - 2. Transformers with different kVA ratings cannot be paralleled.
 - 3. Transformers with the same Z% share load based on their kVA ratings.
 - 4. Higher Z% transformers always carry more load.

Question ID : 441009119641

Option 1 ID : 441009475686

Option 2 ID : 441009475683

Option 3 ID : 441009475684

Option 4 ID : 441009475685

Status : Answered

Chosen Option : 3

Q.26 A circuit has a lagging power factor. To improve the power factor, which of the following devices should be connected and how does it affect the current drawn?

- Ans 1. Resistor in parallel – increases current
2. Capacitor in parallel – reduces current and improves power factor
3. Inductor in parallel – decreases power factor
4. Capacitor in series – improves power factor but increases current

Question ID : 441009159300

Option 1 ID : 441009632071

Option 2 ID : 441009632073

Option 3 ID : 441009632072

Option 4 ID : 441009632074

Status : Answered

Chosen Option : 2

Q.27 In the case of a single line-to-ground fault, the fault current is primarily determined by:

- Ans 1. the zero-sequence impedance of the system
2. the total system impedance, including line and ground impedance
3. the negative-sequence impedance of the system
4. the positive-sequence impedance of the system

Question ID : 44100948896

Option 1 ID : 441009194890

Option 2 ID : 441009194891

Option 3 ID : 441009194889

Option 4 ID : 441009194888

Status : Answered

Chosen Option : 2

Q.28 Why do squirrel-cage induction motors NOT require slip rings?

- Ans 1. They use permanent magnets.
2. They operate at synchronous speed.
3. Rotor bars are short-circuited internally.
4. They require external resistors.

Question ID : 441009109212

Option 1 ID : 441009434568

Option 2 ID : 441009434570

Option 3 ID : 441009434569

Option 4 ID : 441009434571

Status : Answered

Chosen Option : 3

Q.29 In a balanced star-connected three-phase system, the line voltage is 400 V. What is the approximate phase voltage?

- Ans
- 1. 200 V
 - 2. 400 V
 - 3. 230 V
 - 4. 250 V

Question ID : 441009159319

Option 1 ID : 441009632162

Option 2 ID : 441009632159

Option 3 ID : 441009632160

Option 4 ID : 441009632161

Status : Answered

Chosen Option : 3

Q.30 How does increasing the number of digits in a DVM affect its resolution?

- Ans
- 1. It decreases the resolution.
 - 2. It has no effect.
 - 3. It reduces input impedance.
 - 4. It increases the resolution.

Question ID : 441009117443

Option 1 ID : 441009466931

Option 2 ID : 441009466932

Option 3 ID : 441009466933

Option 4 ID : 441009466930

Status : Answered

Chosen Option : 1

Q.31 Why do electrostatic instruments NOT require a separate controlling torque mechanism?

- Ans
- 1. Because they operate on direct current
 - 2. Because damping torque is sufficient
 - 3. Because they use a moving iron system
 - 4. Because the electrostatic force naturally balances the movement

Question ID : 441009120829

Option 1 ID : 441009480354

Option 2 ID : 441009480356

Option 3 ID : 441009480357

Option 4 ID : 441009480355

Status : Answered

Chosen Option : 4

Q.32 The energy density stored in the electric field of an electric dipole is given by:

- Ans
- ✓ 1. $w = \frac{1}{2} \epsilon_0 E^2$
 - ✗ 2. $w = \frac{1}{4} \epsilon_0 E^2$
 - ✗ 3. $w = \frac{1}{2} P \cdot E$
 - ✗ 4. $w = \epsilon_0 E^2$

Question ID : 44100989828

Option 1 ID : 441009357480

Option 2 ID : 441009357479

Option 3 ID : 441009357478

Option 4 ID : 441009357481

Status : Answered

Chosen Option : 3

Q.33 The magnetic field intensity H at a distance r from an infinitely long straight conductor carrying current I is given by:

- Ans
- ✗ 1. $H = \frac{Ir}{2\pi}$
 - ✓ 2. $H = \frac{I}{2\pi r}$
 - ✗ 3. $H = \frac{I}{4\pi r}$
 - ✗ 4. $H = \frac{2\pi I}{r}$

Question ID : 44100989821

Option 1 ID : 441009357452

Option 2 ID : 441009357450

Option 3 ID : 441009357451

Option 4 ID : 441009357453

Status : Answered

Chosen Option : 2

Q.34 In overvoltage protection schemes, what is the primary purpose of the 'voltage transformer' used in the protection circuit?

- Ans
- ✗ 1. To isolate the protection relay from the high voltage system
 - ✗ 2. To measure the line current during a fault
 - ✗ 3. To step down the fault voltage
 - ✓ 4. To provide an accurate representation of the system voltage at a reduced level

Question ID : 44100949714

Option 1 ID : 441009198124

Option 2 ID : 441009198122

Option 3 ID : 441009198121

Option 4 ID : 441009198123

Status : Answered

Chosen Option : 1

Q.35 Which of the following load flow methods uses the bus impedance matrix to solve the system's load flow equations?

- Ans 1. Newton-Raphson Method
 2. Fast Decoupled Load Flow Method
 3. Z-bus or Gauss elimination method
 4. Gauss-Seidel Method

Question ID : 44100948923

Option 1 ID : 441009194993

Option 2 ID : 441009194994

Option 3 ID : 441009194995

Option 4 ID : 441009194992

Status : Answered

Chosen Option : 1

Q.36 Which of the following is a type of controlling system in analogue instruments?

- Ans 1. Electromagnetic control
 2. Thermal control
 3. Spring control
 4. Induction control

Question ID : 441009120045

Option 1 ID : 441009477255

Option 2 ID : 441009477258

Option 3 ID : 441009477256

Option 4 ID : 441009477257

Status : Answered

Chosen Option : 3

Q.37 In Cross Field Theory, the term 'quadrature field' refers to a field that is:

- Ans 1. generated by the capacitor
 2. perpendicular to the stator's main field
 3. opposite in direction to the rotor bars
 4. parallel to the stator's main field

Question ID : 44100995798

Option 1 ID : 441009381151

Option 2 ID : 441009381149

Option 3 ID : 441009381150

Option 4 ID : 441009381148

Status : Answered

Chosen Option : 2

Q.38 For obtaining load commutation in Voltage source inverter, capacitive reactance of load must be _____ its inductive reactance.

- Ans 1. less than
 2. greater than
 3. independent of
 4. equal to

Question ID : 441009153314
Option 1 ID : 441009608423
Option 2 ID : 441009608422
Option 3 ID : 441009608425
Option 4 ID : 441009608424
Status : Answered
Chosen Option : 2

Q.39 Why is standardisation necessary in a DC potentiometer?

- Ans 1. To adjust the power consumption of the circuit
 2. To measure current with high precision
 3. To improve the sensitivity of the instrument
 4. To ensure accuracy by comparing with a known reference voltage

Question ID : 441009117410
Option 1 ID : 441009466793
Option 2 ID : 441009466792
Option 3 ID : 441009466790
Option 4 ID : 441009466791
Status : Answered
Chosen Option : 4

Q.40 An average responding voltmeter is reliable for measuring which type of AC waveform?

- Ans 1. Pulsed DC signals
 2. Distorted waveforms
 3. Pure sine waves
 4. High-frequency signals

Question ID : 441009120126
Option 1 ID : 441009477565
Option 2 ID : 441009477564
Option 3 ID : 441009477563
Option 4 ID : 441009477566
Status : Answered
Chosen Option : 1

Q.41 For a three-phase fault in a balanced power system, the fault current is primarily determined by:

- Ans
- 1. the negative sequence impedance of the system
 - 2. the total system impedance excluding the generator impedance
 - 3. the positive sequence impedance of the system
 - 4. the total system impedance including the ground path

Question ID : 44100948864

Option 1 ID : 441009194765

Option 2 ID : 441009194767

Option 3 ID : 441009194764

Option 4 ID : 441009194766

Status : Answered

Chosen Option : 3

Q.42 In a single-phase half wave circuit with RL load and freewheel diode, freewheel diode conducts only when _____.

- Ans
- 1. SCR is reverse biased
 - 2. SCR is forward biased and conducting
 - 3. supply voltage is positive
 - 4. SCR is forward biased

Question ID : 441009148148

Option 1 ID : 441009588462

Option 2 ID : 441009588463

Option 3 ID : 441009588464

Option 4 ID : 441009588461

Status : Answered

Chosen Option : 1

Q.43 Average load voltage in a buck chopper is given as: (where α is duty cycle of chopper, V_o is output voltage and V_s is supply voltage)

- Ans
- 1. $V_o = \frac{1}{1-\alpha} V_s$
 - 2. $V_o = \frac{1}{1+\alpha} V_s$
 - 3. $V_o = \alpha V_s$
 - 4. $V_o = \frac{1}{\alpha} V_s$

Question ID : 441009150793

Option 1 ID : 441009598422

Option 2 ID : 441009598423

Option 3 ID : 441009598420

Option 4 ID : 441009598421

Status : Answered

Chosen Option : 3

Q.44 The per unit system is used in power system analysis primarily to:

- Ans
- 1. improve the precision of load flow calculations
 - 2. increase the complexity of calculations in the power system
 - 3. maintain consistency in physical units across all calculations
 - 4. simplify the comparison of electrical quantities across different voltage levels

Question ID : 44100948954

Option 1 ID : 441009195114

Option 2 ID : 441009195113

Option 3 ID : 441009195115

Option 4 ID : 441009195112

Status : Answered

Chosen Option : 4

Q.45 In a single-phase capacitor commutated current source inverter with R load, the number of thyristors used are _____.

- Ans
- 1. six
 - 2. two
 - 3. eight
 - 4. four

Question ID : 441009153257

Option 1 ID : 441009608196

Option 2 ID : 441009608194

Option 3 ID : 441009608197

Option 4 ID : 441009608195

Status : Answered

Chosen Option : 3

Q.46 In the following circuit, resistors $R_1 = 2 \Omega$, $R_2 = 4 \Omega$ and $R_3 = 6 \Omega$ are connected in series. The total current flowing through the circuit with a 24 V DC supply is:

- Ans
- 1. 4 A
 - 2. 3 A
 - 3. 2 A
 - 4. 1 A

Question ID : 441009159358

Option 1 ID : 441009632283

Option 2 ID : 441009632284

Option 3 ID : 441009632285

Option 4 ID : 441009632286

Status : Answered

Chosen Option : 3

Q.47 If the population standard deviation is 12 and the sample size is 36, what is the standard error?

Ans 1. 2

2. 3

3. 36

4. 12

Question ID : 441009117062

Option 1 ID : 441009465380

Option 2 ID : 441009465381

Option 3 ID : 441009465379

Option 4 ID : 441009465378

Status : Answered

Chosen Option : 1

Q.48 The electric flux density D at a distance r from a point charge Q is given by:

Ans 1. $D = \frac{Q}{4\pi r^3} \hat{r}$

2. $D = \frac{Q}{4\pi r^2} \hat{r}$

3. $D = \frac{Q}{4\pi \epsilon_0 r^2} \hat{r}$

4. $D = \frac{Q}{4\pi \epsilon r^2} \hat{r}$

Question ID : 44100989805

Option 1 ID : 441009357393

Option 2 ID : 441009357390

Option 3 ID : 441009357391

Option 4 ID : 441009357392

Status : Answered

Chosen Option : 1

Q.49 At the boundary between a conductor and free space, the tangential component of the electric field is:

Ans 1. continuous

2. equal to surface charge density

3. discontinuous

4. zero

Question ID : 44100989368

Option 1 ID : 441009355615

Option 2 ID : 441009355618

Option 3 ID : 441009355616

Option 4 ID : 441009355617

Status : Answered

Chosen Option : 1

Q.50 If the applied voltage in an electro-dynamometer-type voltmeter is doubled, what happens to the deflection?

- Ans
- 1. It doubles
 - 2. It remains the same
 - 3. It becomes four times
 - 4. It decreases by half

Question ID : 441009120396

Option 1 ID : 441009478627

Option 2 ID : 441009478626

Option 3 ID : 441009478628

Option 4 ID : 441009478629

Status : Answered

Chosen Option : 1

Q.51 In the Newton-Raphson method for load flow analysis, the size of the Jacobian matrix for a system with n buses is:

- Ans
- 1. $(2n-2) \times (2n-2)$ matrix
 - 2. $n \times n$ matrix
 - 3. $(n-1) \times (n-1)$ matrix
 - 4. $(2n-1) \times (2n-1)$ matrix

Question ID : 44100948944

Option 1 ID : 441009195074

Option 2 ID : 441009195072

Option 3 ID : 441009195073

Option 4 ID : 441009195075

Status : Answered

Chosen Option : 4

Q.52 In type A chopper, limit of continuous conduction is reached when (Given I_{mn} is initial value of current, I_{mx} is final value of current):

- Ans
- 1. I_{mn} reaches infinity
 - 2. I_{mn} goes to zero
 - 3. I_{mx} reaches infinity
 - 4. I_{mx} goes to zero

Question ID : 441009150742

Option 1 ID : 441009598202

Option 2 ID : 441009598200

Option 3 ID : 441009598203

Option 4 ID : 441009598201

Status : Answered

Chosen Option : 2

Q.53 In a double cage rotor, the outer cage has _____.

- Ans
- 1. lower resistance and smaller cross-sectional area
 - 2. higher resistance and larger cross-sectional area
 - 3. lower resistance and larger cross-sectional area
 - 4. higher resistance and smaller cross-sectional area

Question ID : 441009109318
Option 1 ID : 441009434993
Option 2 ID : 441009434996
Option 3 ID : 441009434995
Option 4 ID : 441009434994
Status : Answered
Chosen Option : 4

Q.54 Type E chopper operates in _____ quadrant(s).

- Ans
- 1. first
 - 2. first and second
 - 3. second
 - 4. all four

Question ID : 441009150837
Option 1 ID : 441009598588
Option 2 ID : 441009598590
Option 3 ID : 441009598589
Option 4 ID : 441009598591
Status : Answered
Chosen Option : 4

Q.55 Which of the following is NOT a characteristic of a transformer?

- Ans
- 1. Operates on alternating current (AC)
 - 2. Changes the frequency of the electrical supply
 - 3. Uses mutual induction between coils
 - 4. Transfers power between circuits without frequency change

Question ID : 441009119859
Option 1 ID : 441009476544
Option 2 ID : 441009476545
Option 3 ID : 441009476546
Option 4 ID : 441009476543
Status : Answered
Chosen Option : 2

Q.56 In an RC circuit, the time constant (τ) is given by:

- Ans 1. R.C
 2. R/C
 3. 1/(RC)
 4. R + C

Question ID : 441009157402
Option 1 ID : 441009624777
Option 2 ID : 441009624776
Option 3 ID : 441009624778
Option 4 ID : 441009624775
Status : Answered
Chosen Option : 1

Q.57 Which of the following semiconductor devices does NOT belong to the thyristor family?

- Ans 1. Programmable unijunction transistor
 2. Silicon unilateral switch
 3. Light activated thyristor
 4. Insulated gate bipolar transistor

Question ID : 441009150982
Option 1 ID : 441009599161
Option 2 ID : 441009599164
Option 3 ID : 441009599163
Option 4 ID : 441009599162
Status : Answered
Chosen Option : 4

Q.58 The electric field at the centre of a uniformly charged circular ring is:

- Ans 1. equal to the charge density of the ring
 2. zero
 3. maximum
 4. minimum

Question ID : 44100989397
Option 1 ID : 441009355734
Option 2 ID : 441009355733
Option 3 ID : 441009355731
Option 4 ID : 441009355732
Status : Answered
Chosen Option : 2

Q.59 The potential V due to a uniform line charge density λ at a distance r (taking reference point r_0) is given by:

- Ans
- 1. $V = \frac{\lambda}{4\pi\epsilon_0 r}$
 - 2. $V = \frac{\lambda}{4\pi\epsilon_0} \ln\left(\frac{r_0}{r}\right)$
 - 3. $V = \frac{\lambda}{2\pi\epsilon_0} \ln r$
 - 4. $V = \frac{\lambda}{\epsilon_0 r}$

Question ID : 44100989529

Option 1 ID : 441009356289

Option 2 ID : 441009356287

Option 3 ID : 441009356288

Option 4 ID : 441009356280

Status : Answered

Chosen Option : 2

Q.60 Which statements about the equivalent circuit of a single-phase induction motor (neglecting core losses) are true?

- I. The magnetising reactance (X_m) is connected in parallel with the rotor circuit only.
- II. Rotor resistance is split into forward and backward components, each equal to $R_r/2$.
- III. Core loss resistance (R_c) is omitted from the circuit.
- IV. Stator impedance includes resistance (R_s) only.

- Ans
- 1. Statement I and II only
 - 2. Statement II and III only
 - 3. Statement III and IV only
 - 4. Statement I and IV only

Question ID : 44100995809

Option 1 ID : 441009399694

Option 2 ID : 441009399695

Option 3 ID : 441009399696

Option 4 ID : 441009399697

Status : Answered

Chosen Option : 3

Q.61 A statically induced EMF occurs when:

- Ans
- 1. the loop and the field move together at the same speed
 - 2. a stationary loop is placed in a changing magnetic field
 - 3. a moving loop cuts through a stationary magnetic field
 - 4. both the loop and the magnetic field remain constant

Question ID : 44100989686

Option 1 ID : 441009356916

Option 2 ID : 441009356913

Option 3 ID : 441009356914

Option 4 ID : 441009356915

Status : Answered

Chosen Option : 2

Q.62 Increasing rotor resistance in a wound-rotor induction motor affects starting torque by

- Ans
- 1. leaving it unchanged
 - 2. eliminating it
 - 3. increasing it
 - 4. decreasing it

Question ID : 441009109181
Option 1 ID : 441009434450
Option 2 ID : 441009434451
Option 3 ID : 441009434449
Option 4 ID : 441009434448
Status : Answered
Chosen Option : 3

Q.63 The real power (P) in an AC circuit is given by:

- Ans
- 1. $P = VI\cos\theta$
 - 2. $P = VI\sin\theta$
 - 3. $P = VI$
 - 4. $P = V/I$

Question ID : 441009157439
Option 1 ID : 441009624923
Option 2 ID : 441009624924
Option 3 ID : 441009624925
Option 4 ID : 441009624926
Status : Answered
Chosen Option : 1

Q.64 In an AC circuit, the power factor is 0.6 lagging. If the active power consumed is 600 W, what is the apparent power?

- Ans
- 1. 1000 VA
 - 2. 400 VA
 - 3. 600 VA
 - 4. 800 VA

Question ID : 441009157448
Option 1 ID : 441009624959
Option 2 ID : 441009624962
Option 3 ID : 441009624961
Option 4 ID : 441009624960
Status : Answered
Chosen Option : 1

Q.65 In the Newton-Raphson method for load flow analysis, the update of voltage magnitudes and angles is performed using:

- Ans
- 1. the Jacobian matrix without any adjustments for power mismatches
 - 2. the direct values of real and reactive power at each bus
 - 3. the inverse of the Jacobian matrix, multiplied by the power mismatches
 - 4. a linear approximation of the power mismatches for each bus

Question ID : 44100948938

Option 1 ID : 441009195051

Option 2 ID : 441009195049

Option 3 ID : 441009195048

Option 4 ID : 441009195050

Status : Answered

Chosen Option : 1

Q.66 What will be the output voltage frequency in a single-phase full wave bridge converter?

- Ans
- 1. Same as input supply frequency
 - 2. Zero
 - 3. Twice the input supply frequency
 - 4. Four times the input supply frequency

Question ID : 441009147833

Option 1 ID : 441009587225

Option 2 ID : 441009587228

Option 3 ID : 441009587226

Option 4 ID : 441009587227

Status : Answered

Chosen Option : 3

Q.67 The balancing equation of the Owen Bridge contains which components?

- Ans
- 1. Inductance, resistance, and capacitance
 - 2. Resistance and inductance
 - 3. Inductance and capacitance
 - 4. Capacitance and resistance

Question ID : 441009116632

Option 1 ID : 441009463756

Option 2 ID : 441009463755

Option 3 ID : 441009463757

Option 4 ID : 441009463758

Status : Answered

Chosen Option : 1

Q.68 Coulomb's law states that the force between two point charges is:

- Ans
- 1. directly proportional to the square of the distance between them
 - 2. independent of the medium in which charges are placed
 - 3. inversely proportional to the product of the charges
 - 4. inversely proportional to the square of the distance between them

Question ID : 44100989395
Option 1 ID : 441009355724
Option 2 ID : 441009355725
Option 3 ID : 441009355726
Option 4 ID : 441009355723
Status : Answered
Chosen Option : 4

Q.69 In a single-phase full wave midpoint converter, _____ commutation is usually employed.

- Ans
- 1. line
 - 2. impulse
 - 3. resonant pulse
 - 4. load

Question ID : 441009147814
Option 1 ID : 441009587157
Option 2 ID : 441009587159
Option 3 ID : 441009587160
Option 4 ID : 441009587158
Status : Answered
Chosen Option : 4

Q.70 Which statements about Star-Star (Y-Y) connections are INCORRECT?

- I. Requires a tertiary delta winding for third-harmonic suppression.
- II. Neutral is available on both primary and secondary sides.
- III. Ideal for heavy unbalanced loads.
- IV. Line voltage = phase voltage.

- Ans
- 1. I and II only
 - 2. II and III only
 - 3. I, III and IV only
 - 4. III and IV only

Question ID : 441009120082
Option 1 ID : 441009477396
Option 2 ID : 441009477397
Option 3 ID : 441009477395
Option 4 ID : 441009477398
Status : Answered
Chosen Option : 4